

LED Test Light

- One LED
- One 470Ω $\frac{1}{2}$ W resistor
- A clicker style pen
- Some wire etc.

