

3 Series, Parallel, and Series-Parallel Circuits

FIGURE 3.4 In a series circuit the voltage is dropped or lowered by each resistance in the circuit. The higher the resistance, the greater the drop in voltage.

PEARSON Advanced Automotive Electricity and Electronics James D. Halperin © 2013 Pearson Higher Education, Inc. Pearson Prentice Hall Upper Saddle River, NJ 07455

3 Series, Parallel, and Series-Parallel Circuits

NOTE: Notice that the voltage drop is proportional to the resistance. In other words, the higher the resistance, the greater the voltage drop. A 6-ohm resistance dropped the voltage three times as much as the voltage drop created by the 2-ohm resistance.

PEARSON Advanced Automotive Electricity and Electronics James D. Halperin © 2013 Pearson Higher Education, Inc. Pearson Prentice Hall Upper Saddle River, NJ 07455

3 Series, Parallel, and Series-Parallel Circuits

FREQUENTLY ASKED QUESTION


Why Check the Voltage Drop Instead of Measuring the Resistance?


Imagine a wire with all strands cut except for one. An ohmmeter can be used to check the resistance of this wire and the resistance would be low, indicating that the wire was okay. But this one small strand cannot properly carry the current currents in the circuit. A voltage drop test is therefore a better test to determine the resistance of components for two reasons:


- An ohmmeter can only test a wire or component that has been disconnected from the circuit and is not carrying current. The resistance rises and then changes when current flows.
- A voltage drop test is a dynamic test because as the current flows through a component, the conductor increases in temperature, which in turn increases resistance. This means that a voltage drop test is testing the circuit during normal operation and is therefore the most accurate way of determining circuit conditions.

A voltage drop test is also easier to perform because the resistance does not have to be known, only that the unwanted loss of voltage in a circuit should be less than 3% or less than about 0.34 volts for any 12-volt circuit.

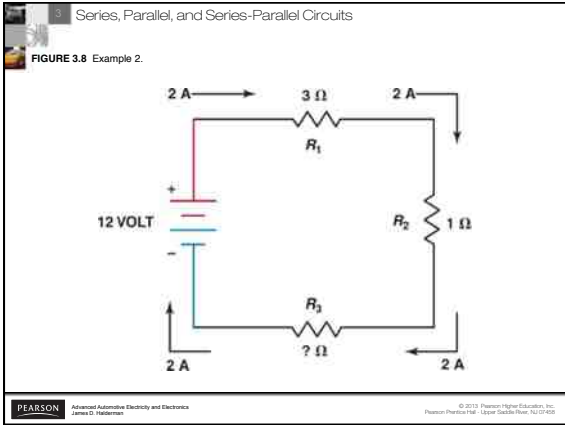PEARSON Advanced Automotive Electricity and Electronics James D. Halperin © 2013 Pearson Higher Education, Inc. Pearson Prentice Hall Upper Saddle River, NJ 07455



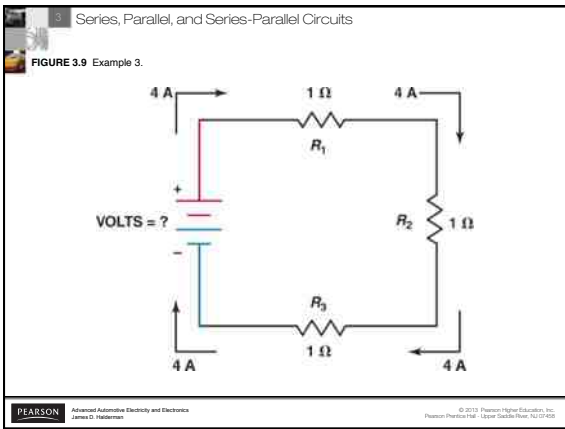

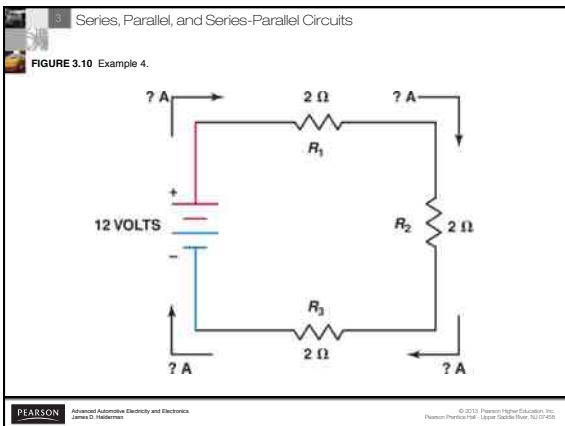

3 Series, Parallel, and Series-Parallel Circuits

FIGURE 3.11 The amount of current flowing into junction point A equals the total amount of current flowing out of the junction.

PEARSON Advanced Automotive Electricity and Electronics James D. Halperin © 2013 Pearson Higher Education, Inc. Pearson Education, Inc., Upper Saddle River, NJ 07458

3 Series, Parallel, and Series-Parallel Circuits

NOTE: A parallel circuit drops the voltage from source voltage to zero (ground) across the resistance in each leg of the circuit.

PEARSON Advanced Automotive Electricity and Electronics James D. Halperin © 2013 Pearson Higher Education, Inc. Pearson Education, Inc., Upper Saddle River, NJ 07458

3 Series, Parallel, and Series-Parallel Circuits

FIGURE 3.12 The current in a parallel circuit splits (divides) according to the resistance in each branch.

PEARSON Advanced Automotive Electricity and Electronics James D. Halperin © 2013 Pearson Higher Education, Inc. Pearson Education, Inc., Upper Saddle River, NJ 07458

3 Series, Parallel, and Series-Parallel Circuits

TECH TIP

The Path of Least Resistance

There is an old saying that electricity will always take the path of least resistance. This is true, especially if there is a fault such as in the secondary (high-voltage) section of the ignition system. If there is a path to ground that is lower than the path to the spark plug, the high-voltage spark will take the path of least resistance. In a parallel circuit where there is more than one path for the current to flow, most of the current will flow through the branch with the lower resistance. This does not mean that all of the current will flow through the lowest resistance, because the other path does provide a path to ground, and the amount of current flow through the other branches is determined by the resistance and the applied voltage according to Ohm's law.

PEARSON Advanced Automotive Electricity and Electronics James D. Halperin © 2013 Pearson Higher Education, Inc. Pearson Periodicals, Upper Saddle River, NJ 07088

3 Series, Parallel, and Series-Parallel Circuits


NOTE: Determining the total resistance of a parallel circuit is very important in automotive service. Electronic fuel-injector and diesel engine glow plug circuits are two of the most commonly tested circuits where parallel circuit knowledge is required. Also, when installing extra lighting, the technician must determine the proper gauge wire and protection device.

PEARSON Advanced Automotive Electricity and Electronics James D. Halperin © 2013 Pearson Higher Education, Inc. Pearson Periodicals, Upper Saddle River, NJ 07088

3 Series, Parallel, and Series-Parallel Circuits

FIGURE 3.13 In a typical parallel circuit, each resistance has power and ground and each leg operates independently of the other legs of the circuit.

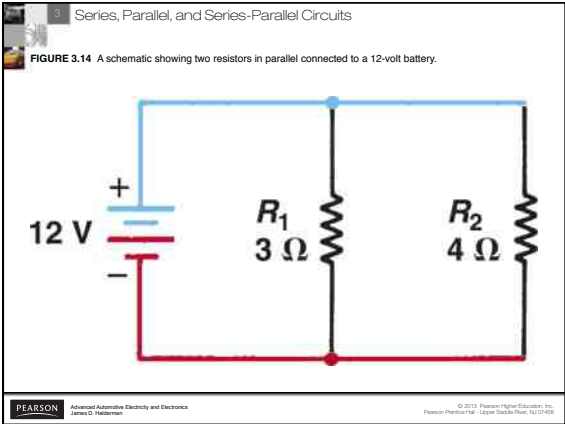
PEARSON Advanced Automotive Electricity and Electronics James D. Halperin © 2013 Pearson Higher Education, Inc. Pearson Periodicals, Upper Saddle River, NJ 07088



3 Series, Parallel, and Series-Parallel Circuits

NOTE: Which resistor is R_1 and which is R_2 is not important. The position in the formula makes no difference in the multiplication and addition of the resistor values.

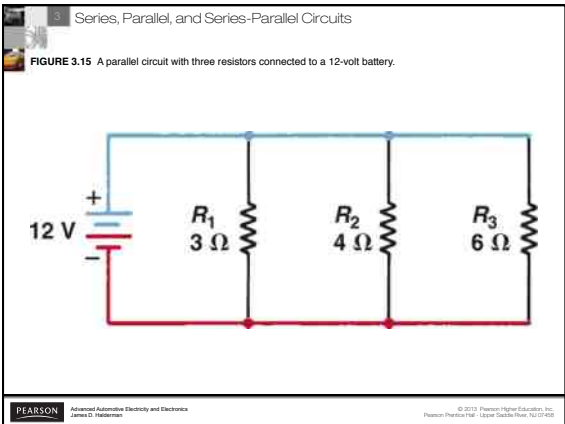PEARSON Advanced Automotive Electricity and Electronics James D. Halperin © 2013 Pearson Higher Education, Inc. Pearson Education, Inc. Upper Saddle River, NJ 07083



3 Series, Parallel, and Series-Parallel Circuits

FIGURE 3.18 A parallel circuit containing four 12-ohm resistors. When a circuit has more than one resistor of equal value, the total resistance can be determined by simply dividing the value of the resistance (12 ohms in this example) by the number of equal-value resistors (4 in this example) to get 3 ohms.

PEARSON Advanced Automotive Electricity and Electronics James D. Halperin © 2013 Pearson Higher Education, Inc. Pearson Prentice-Hall, Upper Saddle River, NJ 07458

3 Series, Parallel, and Series-Parallel Circuits

NOTE: Since most automotive and light-truck electrical circuits involve multiple use of the same resistance, this method is the most useful. For example, if six additional 12-ohm lights were added to a vehicle, the additional lights would represent just 2 ohms of resistance ($12 \Omega / 6 \text{ lights} = 2$). Therefore, 6 amperes of additional current would be drawn by the additional lights ($I = E/R = 12 \text{ V} / 2 \Omega = 6 \text{ A}$).

PEARSON Advanced Automotive Electricity and Electronics James D. Halperin © 2013 Pearson Higher Education, Inc. Pearson Prentice-Hall, Upper Saddle River, NJ 07458

3 Series, Parallel, and Series-Parallel Circuits

FIGURE 3.19 Example 1.

PEARSON Advanced Automotive Electricity and Electronics James D. Halperin © 2013 Pearson Higher Education, Inc. Pearson Prentice-Hall, Upper Saddle River, NJ 07458

