

Automotive Electrical & Engine Performance 7/E














Chapter 5 Series, Parallel, & Series Parallel Circuits










Opening Your Class









KEY ELEMENT	EXAMPLES
Introduce Content	This course or class covers Automotive Electrical & Engine Performance . It correlates material to task lists specified by ASE and NATEF.
Motivate Learners	Explain how the knowledge of how something works translates into the ability to use that knowledge to figure why the engine does not work correctly and how this saves diagnosis time, which translates into more money.
State the learning objectives for the chapter or course you are about to cover and explain this is what they should be able to do as a result of attending this session or class.	<p>Explain the chapter learning objectives to the students.</p> <ol style="list-style-type: none">1. Identify a series circuit.2. Identify a parallel circuit.3. Identify a series-parallel circuit.4. Calculate the total resistance in a parallel circuit.5. State Kirchhoff's voltage law.6. Calculate voltage drops in a series circuit.7. Explain series and parallel circuit laws.8. State Kirchhoff's current law.9. Identify where faults in a series-parallel circuit can be detected or determined. <p>Prepare for ASE Electrical/Electronic Systems (A6) certification test content area "A" (General Electrical/ Electronic System Diagnosis).</p>
Establish the Mood or Climate	Provide a <i>WELCOME</i> , Avoid put downs and bad jokes.
Complete Essentials	Restrooms, breaks, registration, tests, etc.
Clarify and Establish Knowledge Base	Do a round robin of the class by going around the room and having each student give their backgrounds, years of experience, family, hobbies, career goals, or anything they want to share.











NOTE: This lesson plan is based on Automotive Electrical & Engine Performance 7/E Chapter Images found on Jim's web site @ www.jameshalderman.com











LINK CHP 5: [Chapter Images](#)










ICONS	Ch05 ELECTRICAL CIRCUITS
          <p data-bbox="354 1346 456 1367">QUESTION</p> <p data-bbox="204 1373 526 1430">KIRCHHOFF'S VOLTAGE LAW</p>  <p data-bbox="220 1486 329 1528">DEMO</p>  	<p data-bbox="623 302 1279 380">1. SLIDE 1 CH5 SERIES, PARALLEL, & SERIES-PARALLEL CIRCUITS</p> <p data-bbox="623 396 1414 428">2. SLIDES 2-3 EXPLAIN OBJECTIVES & KEY TERMS</p> <p data-bbox="623 443 1390 558">Check for ADDITIONAL VIDEOS & ANIMATIONS @ http://www.jameshalderman.com/ WEB SITE IS CONSTANTLY UPDATED</p> <p data-bbox="583 716 1406 863">At the beginning of this class, you can download the crossword puzzle & Word Search from the links below to familiarize your class with the terms in this chapter & then discuss them</p> <p data-bbox="623 884 1292 915"><u>Crossword Puzzle (Microsoft Word) (PDF)</u></p> <p data-bbox="623 930 1328 961"><u>Word Search Puzzle (Microsoft Word) (PDF)</u></p> <p data-bbox="623 1016 1390 1226">2. SLIDE 2 EXPLAIN Figure 5-1 Series circuit with 3 bulbs. All current flows through all resistances (bulbs). Total resistance of circuit is sum of total resistance of bulbs, & bulbs will light dimly because of increased resistance & reduction of current flow (amperes) through circuit.</p> <p data-bbox="583 1241 1406 1430"><u>DISCUSSION: DISCUSS SERIES CIRCUITS. WHERE, AND FOR WHAT PURPOSE, ARE SERIES CIRCUITS USED? REVIEW OHM'S LAW FOR USE IN UNDERSTANDING SERIES CIRCUITS. WHY IS TOTAL RESISTANCE SUM OF ALL RESISTANCES?</u></p> <p data-bbox="583 1444 1398 1514"><u>DEMONSTRATION: SET-UP CIRCUIT IN FIGURE 5-1 & SHOW STUDENTS HOW TO USE</u></p> <p data-bbox="623 1589 1341 1656">3. SLIDE 3 EXPLAIN Figure 5-2 series circuit with 2 bulbs.</p> <p data-bbox="623 1766 927 1797">EXPLAIN TECH TIP</p>

ICONS	Ch05 ELECTRICAL CIRCUITS
	4. SLIDE 4 EXPLAIN Figure 5-3 As current flows through a circuit, voltage drops in proportion to amount of resistance in circuit. Most, if not all, of resistance should occur across load such as bulb in circuit. All of other components & wiring should produce little, if any, voltage drop. If a wire or connection did cause a voltage drop, less voltage would be available to light bulb and bulb would be dimmer than normal.
	5. SLIDE 5 EXPLAIN Figure 5-4 In a series circuit voltage is dropped or lowered by each resistance in the circuit. Higher resistance, greater drop in voltage.
	6. SLIDE 6 EXPLAIN Figure 5-5 Voltmeter reads differences of voltage between test leads. Voltage read across a resistance is the voltage drop that occurs when current flows through a resistance. A voltage drop is also called an “IR” drop because it is calculated by multiplying the current (I) through the resistance (electrical load) by the value of the resistance (R).
	KIRCHHOFF'S VOLTAGE LAW: 2ND LAW: VOLTAGE AROUND ANY CLOSED CIRCUIT IS EQUAL TO THE SUM (TOTAL) OF THE VOLTAGE DROPS ACROSS THE RESISTANCES
	<u>DISCUSSION:</u> HAVE STUDENTS DISCUSS KIRCHHOFF'S SECOND VOLTAGE LAW. HOW DOES KIRCHHOFF'S LAW RELATE TO OHM'S LAW?
	DISCUSS FREQUENTLY ASKED QUESTION
	7. SLIDE 7 EXPLAIN Figure 5-6 In this series circuit with a 2-ohm resistor and a 4-ohm resistor, current (2 amperes) is same throughout even though voltage drops across each resistor.
	<u>COMPLETE SERIES CIRCUIT WORKSHEETS 1, 2, & 3 TASK SHEET ON ELECTRICAL CIRCUITS</u>
	<u>Math Formula, Series Circuit Resistance (View) (Download)</u> <u>Series Circuit, Open Circuit (View) (Download)</u>

ICONS	Ch05 ELECTRICAL CIRCUITS
	<p>TASK: HAVE STUDENTS PERFORM EXPERIMENTS ON SERIES CIRCUITS: CONSTRUCT A CIRCUIT SIMILAR TO ONE IN FIGURE 5-4. SHOW STUDENTS HOW TO CHECK VOLTAGE DROP AT EACH LAMP. ASK THEM TO ADD UP VOLTAGE DROPS & COMPARE THEM TO SOURCE VOLTAGE.</p>
	<p>TASK: HAVE STUDENTS PERFORM EXPERIMENTS ON SERIES CIRCUITS CONSTRUCT A CIRCUIT SIMILAR TO ONE IN FIGURE 5-8, FIGURE 5-9, & FIGURE 5-10. WHY DOES CURRENT REMAIN CONSTANT, EVEN THOUGH THERE ARE DIFFERENT RESISTANCES?</p>
	<p>HOMEWORK: SEARCH INTERNET:: RESEARCH 2 OR MORE APPLICATIONS OF SERIES CIRCUITS. ASK THEM TO DRAW CONCLUSIONS ABOUT SETTINGS IN WHICH SERIES CIRCUITS ARE USED & WHY ANOTHER TYPE OF CIRCUIT IS NOT USED.</p>
	<p>8. SLIDE 8 EXPLAIN Figure 5-7 Example 1. 9. SLIDE 9 EXPLAIN Figure 5-8 Example 2. 10. SLIDE 10 EXPLAIN Figure 5-9 Example 3. 11. SLIDE 11 EXPLAIN Figure 5-10 Example 4.</p>
	<p>12. SLIDE 12 EXPLAIN Figure 5-11 amount of current flowing into junction point A equals the total amount of current flowing out of the junction</p>
<p>Kirchhoff's Current Law: 1st LAW: Current flowing into any junction of circuit equal to current flowing out of junction</p>	
 	<p>DEMONSTRATION: BUILD PARALLEL CIRCUIT IN FIGURE 5-11. SHOW WHAT HAPPENS WHEN 1 BULB IS REMOVED. ASK THEM TO COMPARE THIS CIRCUIT WITH SERIES CIRCUIT. CONSTRUCT SERIES & PARALLEL CIRCUIT, EACH WITH 3 IDENTICAL BULBS. MEASURE TOTAL RESISTANCE IN EACH CIRCUIT. <u>ASK:</u> HOW DO PARALLEL CIRCUITS COMPARE TO SERIES CIRCUITS?</p>
	<p>Parallel Circuit, Open (View) (Download) Parallel Circuits, Volts (View) (Download) Parallel Circuit (View) (Download)</p>

ICONS	Ch05 ELECTRICAL CIRCUITS
	<p>13. SLIDE 13 EXPLAIN Figure 5-12 current in a parallel circuit splits (divides) according to resistance in each branch</p>
	<p>EXPLAIN TECH TIP</p>
	<p>14. SLIDE 14 EXPLAIN Figure 5-13 In a typical parallel circuit, each resistance has power and ground and each leg operates independently of other legs of circuit</p>
	<p>DEMO BUILD FIGURE 5-13: SHOW HOW TO SOLVE FOR TOTAL CIRCUIT CURRENT. CHANGE VALUES AND HAVE STUDENTS SOLVE FOR CURRENT FLOW</p>
	<p>15. SLIDE 15 EXPLAIN Figure 5-14 Schematic showing 2 resistors in parallel connected to 12-volt battery.</p>
	<p>DEMONSTRATE BUILDING PARALLEL CIRCUITS, USING FIGURES: 5-13, 5-14, & 5-15</p>
	<p>BUILD FIGURE 5-14: CALCULATE RESISTANCE OF FIGURE 5-14 USING. CHANGE VALUES & HAVE STUDENTS SOLVE FOR RESISTANCE.</p>
	<p>16. SLIDE 16 EXPLAIN Figure 5-15 parallel circuit with three resistors connected to a 12-volt battery.</p>
	<p>BUILD FIGURE 5-15: CALCULATE RESISTANCE OF FIGURE 5-15. CHANGE VALUES & HAVE STUDENTS SOLVE FOR RESISTANCE.</p>
	<p>17. SLIDE 17 EXPLAIN Figure 5-16 Using an electronic calculator to determine total resistance of parallel circuit.</p>

ICONS	Ch05 ELECTRICAL CIRCUITS
	<p>DEMONSTRATION: SHOW STUDENTS HOW TO SOLVE PROBLEM IN FIGURE 5-16 USING CALCULATOR. HAVE STUDENTS WORK WITH YOU AS YOU SOLVE PROBLEM</p>
	<p>HANDS-ON TASK: STUDENTS WORK IN TEAMS & USE CALCULATOR TO SOLVE PARALLEL CIRCUIT PROBLEMS USING FIGURE 5-16</p>
	<p>18. SLIDE 18 EXPLAIN Figure 5-17 Another example of how to use an electronic calculator to determine the total resistance of a parallel circuit. The answer is 13.45 ohms. Notice that the effective resistance of this circuit is less than the resistance of the lowest branch (20 ohms).</p>
	<p>19. SLIDE 19 EXPLAIN Figure 5-18 A parallel circuit containing four 12-ohm resistors. When a circuit has more than one resistor of equal value, the total resistance can be determined by simply dividing the value of the resistance (12 ohms in this example) by the number of equal-value resistors (4 in this example) to get 3 ohms</p>
	<p>DISCUSSION: ASK STUDENTS TO TALK ABOUT METHODS FOR SOLVING PARALLEL CIRCUIT PROBLEMS. WHICH METHOD IS EASIEST TO USE?</p>
 	<p>20. SLIDE 20 EXPLAIN Figure 5-19 Example 1. 21. SLIDE 21 EXPLAIN Figure 5-20 Example 2. 22. SLIDE 22 EXPLAIN Figure 5-21 Example 3. 23. SLIDE 23 EXPLAIN Figure 5-22 Example 4.</p>
	<p>TASK: BUILD PARALLEL CIRCUITS IN FIGURES 5-19, 5-20, 5-21, & 5-22. DETERMINE WHAT THEY ARE TO SOLVE FOR.</p>
	<p>DISCUSSION: ASK STUDENTS TO TALK ABOUT VOLTAGE IN PARALLEL CIRCUITS. IS VOLTAGE ALWAYS 12 VOLTS? EXPLAIN THAT THE VOLTAGE IN AUTOMOTIVE APPLICATIONS OF PARALLEL CIRCUITS USUALLY IS 12 VOLTS, BUT THAT THE SAME RULES WOULD APPLY IF VOLTAGE WERE 20, 30, OR 50 VOLTS OR MORE.</p>
	<p>COMPLETE PARALLEL CIRCUIT WORKSHEETS 1, 2, & 3 TASK SHEET ON ELECTRICAL CIRCUITS</p>

ICONS	Ch05 ELECTRICAL CIRCUITS
	HOMEWORK:: CHANGE VALUES FOR FIGURES 5–16 & 5–17 AND HAVE THE STUDENTS SOLVE FOR RESISTANCE. GRADE STUDENTS ON THEIR UNDERSTANDING OF CIRCUITS AND METHODS FOR SOLVING THE PROBLEMS, AS WELL AS ACCURATE CALCULATIONS.
	<p>24. SLIDE 24 EXPLAIN Figure 5-23 series-parallel circuit.</p> <p>25. SLIDE 25 EXPLAIN Figure 5-24 complete headlight circuit with all bulbs & switches is series-parallel circuit.</p>
	DISCUSSION: DISCUSS 3 USE OF SERIES-PARALLEL CIRCUITS IN AUTOMOTIVE WIRING SYSTEMS. WHAT ARE SERIES CONNECTIONS AND WHAT ARE THE PARALLEL CONNECTIONS FOR HEADLIGHT SWITCH?
	DEMONSTRATION: BUILD SERIES-PARALLEL CIRCUITS ON PROJECT BOARD IN FIGURES 5-26 AND 5-27 & SHOW STUDENTS HOW TO SOLVE THE PROBLEMS
	<p>26. SLIDE 26 EXPLAIN Figure 5-25 Solving series-parallel circuit problem.</p>
	<p>27. SLIDE 27 EXPLAIN Figure 5-26 Example 1.</p> <p>28. SLIDE 28 EXPLAIN Figure 5-27 Example 2.</p> <p>29. SLIDE 29 EXPLAIN Figure 5-28 Example 3.</p> <p>30. SLIDE 30 EXPLAIN Figure 5-29 Example 4.</p>
	TRAINER TASK: BUILD SERIES-PARALLEL CIRCUITS IN FIGURES 5-28 & 5-29
	COMPLETE SERIES-PARALLEL CIRCUIT WORKSHEETS 1, 2, & 3 TASK SHEET
	HOMEWORK: SEARCH INTERNET HAVE STUDENTS USE INTERNET TO RESEARCH WIRING DIAGRAMS. ASK THEM TO DOWNLOAD AT LEAST 2 WIRING DIAGRAMS TO COMPARE AND CONTRAST