

FIGURE 21-1 A typical TP sensor mounted on the throttle plate of this port-injected engine.



---

---

---

---


---

---

---

---

FIGURE 21-2 The signal voltage from a throttle position increases as the throttle is opened because the wiper arm is closer to the 5-volt reference. At idle, the resistance of the sensor winding effectively reduces the signal voltage output to the computer.

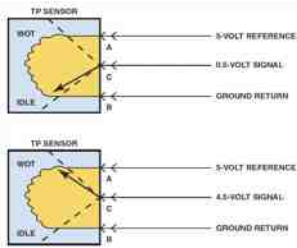

---

---

---

---

---

---

---

---

FIGURE 21-3 A meter lead connected to a T-pin that was gently pushed along the signal wire of the TP sensor until the point of the pin touched the metal terminal inside the plastic connector.



---

---

---

---


---

---

---

---

**FIGURE 21-4** A typical waveform of a TP sensor signal as recorded on a DSO when the accelerator pedal was depressed with the ignition switch on (engine off). Clean transitions and the lack of any glitches in this waveform indicate a good sensor. (Courtesy of Fluke Corporation)

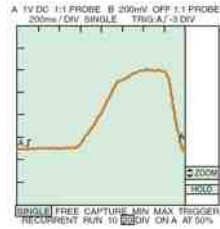

---

---

---

---

---

---

---

---

**FIGURE 21-5** Checking the 5-volt reference from the computer being applied to the TP sensor with the ignition switch on (engine off).



---

---

---

---

---

---

---

---

**FIGURE 21-6** Checking the voltage drop between the TP sensor ground and a good engine ground with the ignition on (engine off). A reading of greater than 0.2 volt (200 mV) represents a bad computer ground.



---

---

---

---

---

---

---

---