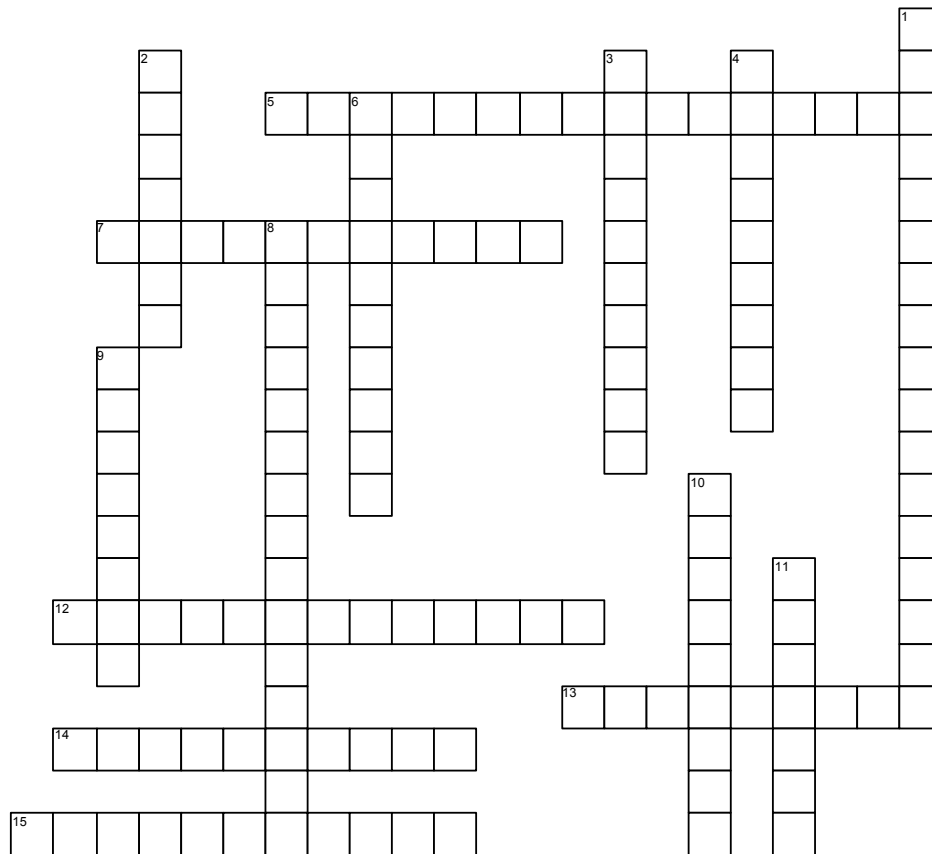


Series Circuits

Chapter 5



<http://jameshaldeman.com>

ACROSS

- 5 Most vehicles are equipped with a method of dimming the brightness of the dash lights by turning a _____.
- 7 _____ almost seems to act as if it knows what resistances are ahead on the long trip through a circuit.
- 12 A _____ is a complete circuit that has only one path for current to flow through all of the electrical loads.
- 13 If a circuit has little or no resistance, then as many _____ as possible attempt to flow through the complete circuit.
- 14 The circuit must be continuous without any breaks, this is called _____.
- 15 A _____ is the amount of electrical pressure required to push electrons through a resistance.

DOWN

- 1 Electrical loads or resistance connected in series behave following _____.
- 2 Voltage drop can be determined by using _____ and calculating for voltage using the value of each resistance individually.
- 3 Any resistance in a circuit causes the voltage to drop in _____ to the amount of the resistance.
- 4 His voltage law states: The voltage around any closed circuit is equal to the sum of the voltage drops across the resistances.
- 6 A series circuit is a circuit containing more than one _____ in which all current must flow through in the circuit.
- 8 The _____ in a series circuit is the sum total of the individual resistances.
- 9 An _____ can only test a wire or component that has been disconnected from the circuit and is not carrying current.
- 10 A German _____, Gustav Robert Kirchhoff developed laws about electrical circuits.
- 11 Because an electrical load needs both a power and a ground to operate, a break anywhere in a series circuit will cause the _____ in the circuit to stop.