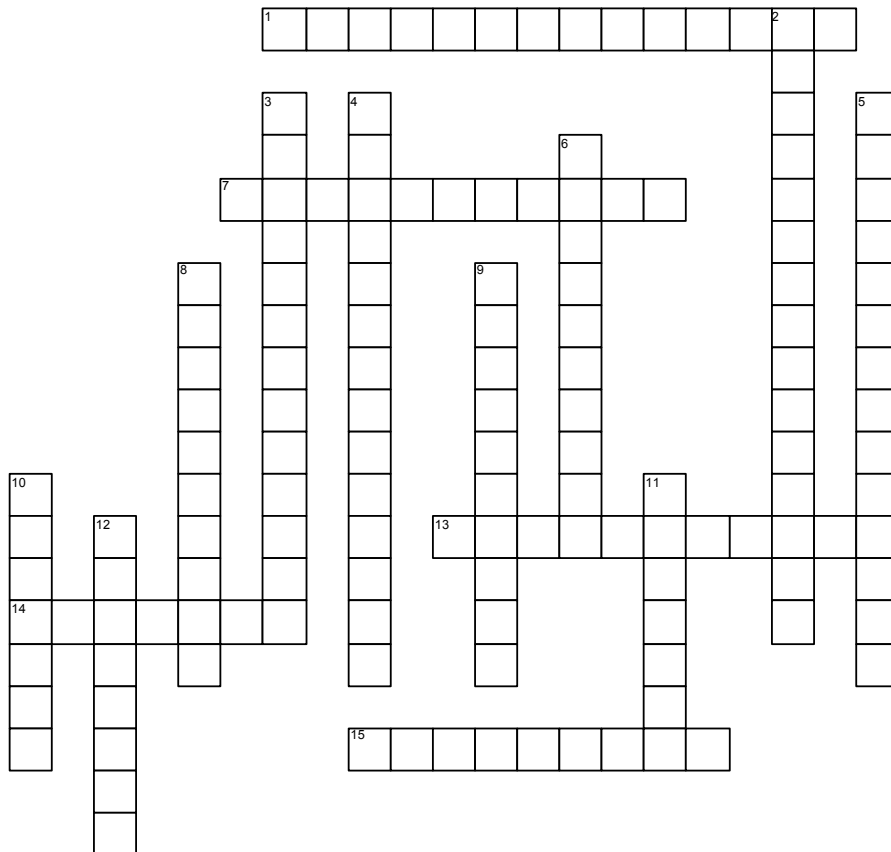


# Electrical Circuits

## Chapter 21



<http://jameshalderman.com>

### ACROSS

- 1 \_\_\_\_\_ can be caused by corroded connections or sockets.
- 7 A vehicle's battery is an example of a \_\_\_\_\_.
- 13 An \_\_\_\_\_ is any circuit that is not complete, or that lacks continuity, such as a broken wire.
- 14 If a wire or component is shorted to voltage, it is commonly referred to as being \_\_\_\_\_.
- 15 The path from the power source to the load is called the \_\_\_\_\_.

### DOWN

- 2 Every \_\_\_\_\_ contains a power source, protection, power path, electrical load, and return path.
- 3 A \_\_\_\_\_ is a type of short circuit that occurs when the current bypasses part of the normal circuit and flows directly to ground.
- 4 A light bulb or electric motor are examples of an \_\_\_\_\_.
- 5 A \_\_\_\_\_ occurs when the power side of one circuit is electrically connected to the power side of another circuit.
- 6 A fuse or circuit breaker are examples of circuit \_\_\_\_\_.
- 8 A circuit that is continuous throughout is said to have \_\_\_\_\_.
- 9 The \_\_\_\_\_ is another name for the ground path.
- 10 \_\_\_\_\_ states it requires 1 volt to push 1 ampere through 1 ohm of resistance.
- 11 A \_\_\_\_\_ is a complete path that electrons travel from a power source through a load and back to the power source.
- 12 A defective component or circuit that is shorted to ground is commonly called \_\_\_\_\_.