

# Maintenance and Light Repair Workbook Chapter 24

Name: \_\_\_\_\_ Class \_\_\_\_\_ Date: \_\_\_\_\_  
Instructor: \_\_\_\_\_ Textbook Pages 276 – 281

Answer the questions and identify the page number that the answer was found in the textbook

1. A \_\_\_\_\_ is a complete path that electrons travel from a power source (such as a battery) through a load such as a light bulb and back to the power source. Page \_\_\_\_
  - A. course
  - B. watt
  - C. circuit
  - D. diagram
  
2. An \_\_\_\_\_ is any circuit that is *not* complete, or that lacks continuity, such as a broken wire. Page \_\_\_\_
  
3. High resistance can be caused by any of the following *except*:
  - A. Corroded connections or sockets
  - B. Loose terminals in a connector
  - C. Loose ground connections
  - D. Worn Insulation
  
4. For *any* electrical circuit to work at all, it must be continuous from the \_\_\_\_\_ through all the wires and components, and back to the \_\_\_\_\_. Page \_\_\_\_
  
5. \_\_\_\_\_ current will flow through an open circuit. Page \_\_\_\_
  - A. Little
  - B. High
  - C. No
  - D. Direct

6. A \_\_\_\_\_ in a vehicle is an example of devices that open a circuit to control its operation. Page \_\_\_\_\_

- A. wiper motor
- B. horn
- C. headlight switch
- D. light bulb

7. A \_\_\_\_\_ is a type of short circuit that occurs when the current bypasses part of the normal circuit and flows directly to ground. Page \_\_\_\_\_

8. If there is high resistance anywhere in a circuit, it may cause all the following problems *except*: Page \_\_\_\_\_

- A. Slow operation of a motor-driven unit, such as the windshield wipers or blower motor
- B. Dim lights
- C. Excessively bright lights
- D. No operation of a circuit or electrical component

9. \_\_\_\_\_ can also be known as Electromotive force. Page \_\_\_\_\_

10. What circuit failure will most likely cause a fuse to blow? Page \_\_\_\_\_

- A. Short to voltage
- B. Short to ground
- C. High resistance
- D. Open