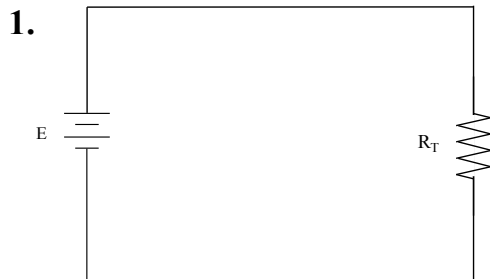


Series Circuit Worksheet #1


Meets NATEF Task: (A6-A-2) Diagnose electrical/electronic integrity for series, parallel, and series-parallel circuits using principles of electricity. (Ohm's Law).

Name _____ Date _____ Time on Task _____


Make/Model _____ Year _____ Evaluation: 4 3 2 1



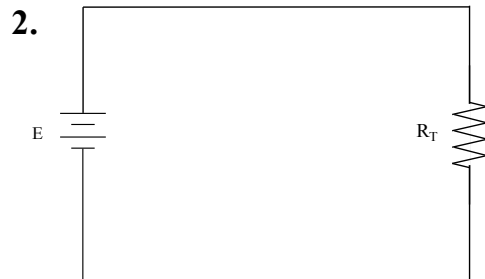
$E = 12 \text{ volts}$
 $I_T = 3 \text{ amperes}$
 $R_T = \underline{\hspace{2cm}}$



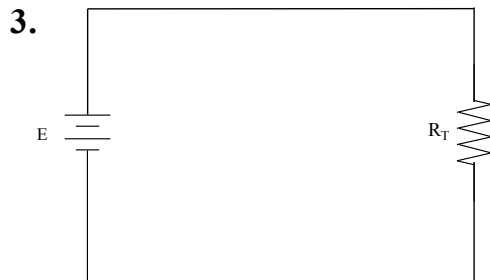
$E = 12 \text{ volts}$
 $I_T = \underline{\hspace{2cm}}$
 $R_T = 3 \text{ ohms}$



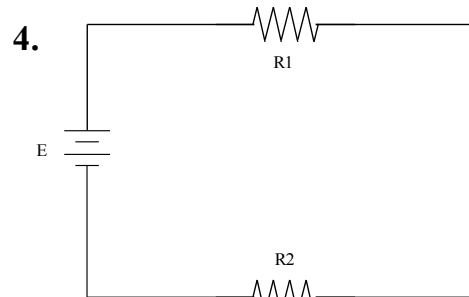
$E = \underline{\hspace{2cm}}$
 $I_T = 3 \text{ amperes}$
 $R_T = 4 \text{ ohms}$



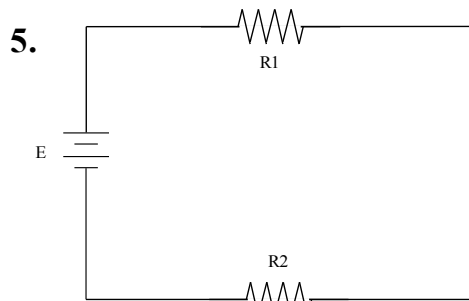$E = 12 \text{ volts}$
 $I_T = \underline{\hspace{2cm}}$
 $R1 = 1 \text{ ohm}$
 $R2 = 1 \text{ ohm}$



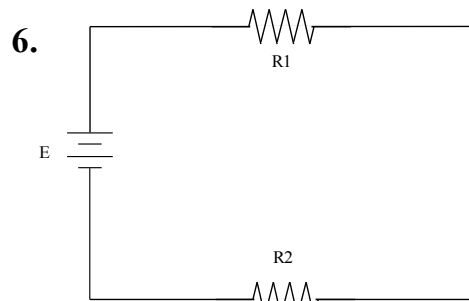$E = \underline{\hspace{2cm}}$
 $I_T = 2 \text{ amperes}$
 $R1 = 3 \text{ ohms}$
 $R2 = 3 \text{ ohms}$



$E = 12 \text{ volts}$
 $I_T = 3 \text{ amperes}$
 $R1 = 3 \text{ ohms}$
 $R2 = \underline{\hspace{2cm}}$