

# Power Accessory Diagnosis

**Meets NATEF Task:** (A6-H-1, A6-H-2, A6-H-3) Diagnose motor-driven accessory circuits; determine necessary action. (P-2, P-3, P-2)

Name \_\_\_\_\_ Date \_\_\_\_\_ Time on Task \_\_\_\_\_

Make/Model/Year \_\_\_\_\_ VIN \_\_\_\_\_ Evaluation: 4 3 2 1

\_\_\_\_\_ 1. Check service information for specified testing procedures to diagnose fault(s) in the power accessory systems.

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_ 2. Locate the power window schematics and determine the following information.

a. Describe the location of the power window master control switch \_\_\_\_\_

\_\_\_\_\_

b. Describe the location of the rear defogger relay \_\_\_\_\_

\_\_\_\_\_

c. Describe the location of the cruise control servo unit (if equipped) \_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_ 3. Describe the specified testing procedure (major steps)

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_ 4. Describe the ground(s) for the power windows.

\_\_\_\_\_

\_\_\_\_\_



\_\_\_\_\_ 5. Based on the inspection and test results, what is the necessary action? \_\_\_\_\_

\_\_\_\_\_