


Parallel Circuit Worksheet #2

Meets ASE Task: (A6-A-2) P-1 Diagnose electrical/electronic integrity for series, parallel, and series-parallel circuits using principles of electricity (Ohm's Law).

Name _____ Date _____ Time on Task _____


Make/Model/Year _____ VIN _____ Evaluation: 4 3 2 1

1.

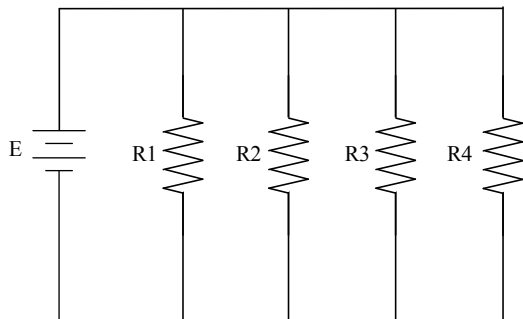


$$\begin{array}{ll} E = 12 \text{ volts} & R1 = 4 \text{ ohms} \\ I_T = \underline{\hspace{1cm}} & R2 = 12 \text{ ohms} \\ R1 = 4 \text{ ohms} & R4 = 12 \text{ ohms} \end{array}$$

2.

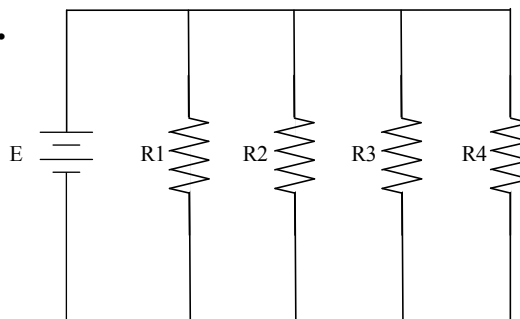


$$\begin{array}{ll} E = \underline{\hspace{1cm}} & R1 = 12 \text{ ohms} \\ I_T = 4 \text{ amperes} & R2 = 12 \text{ ohms} \\ R1 = 12 \text{ ohms} & R3 = 12 \text{ ohms} \end{array}$$

3.

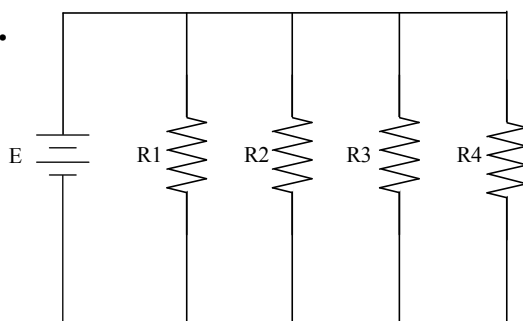


$$\begin{array}{ll} E = \underline{\hspace{1cm}} & R2 = 4 \text{ ohms} \\ I_T = 1 \text{ ampere} & R3 = 6 \text{ ohms} \\ R1 = 2 \text{ ohms} & R4 = 12 \text{ ohms} \end{array}$$

4.

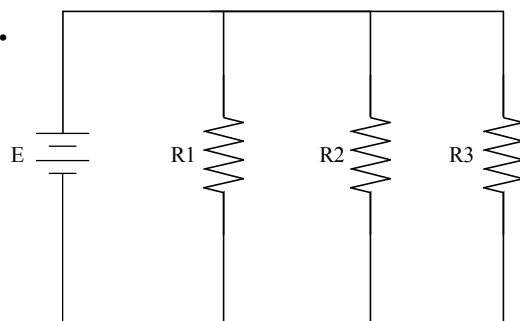


$$\begin{array}{ll} E = 12 \text{ volts} & R2 = 8 \text{ ohms} \\ I_T = \underline{\hspace{1cm}} & R3 = 4 \text{ ohms} \\ R1 = 8 \text{ ohms} & \end{array}$$

5.

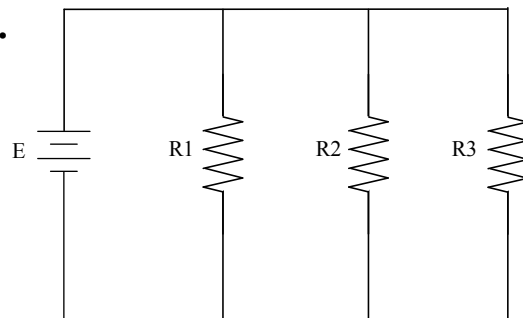

$$\begin{array}{ll} E = 12 \text{ volts} & R2 = 12 \text{ ohms} \\ I_T = 4 \text{ amperes} & R3 = \underline{\hspace{1cm}} \\ R1 = 12 \text{ ohms} & \end{array}$$

6.

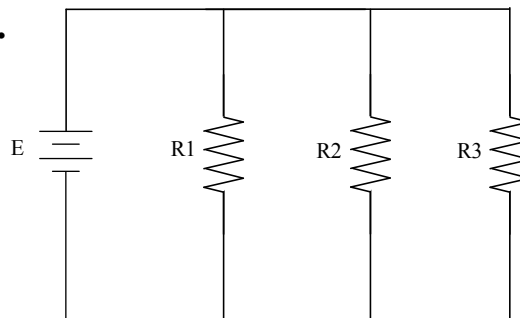

$$\begin{array}{ll} E = \underline{\hspace{1cm}} & R2 = 24 \text{ ohms} \\ I_T = 2 \text{ amperes} & R3 = 12 \text{ ohms} \\ R1 = 24 \text{ ohms} & \end{array}$$