



Electrical Circuits

Meets NATEF Task: Not specified by NATEF

Name _____ Date _____ Time on Task _____

Make/Model/Year _____ VIN _____ Evaluation: 4 3 2 1

_____ 1. Draw a complete electrical circuit and label all of the parts.

_____ 2. What is an open circuit? _____

_____ 3. Describe the difference between a short-to-voltage and a short-to-ground. _____

_____ 4. State Ohm's Law _____

_____ 5. State Watt's Law _____
