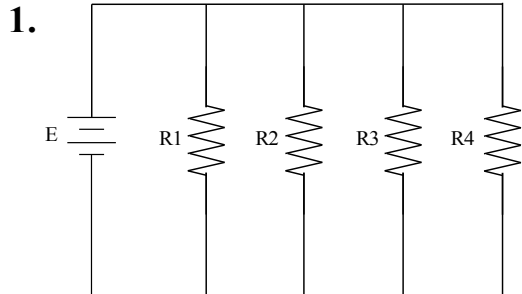


Parallel Circuit Worksheet #2


Meets NATEF Task: (A6-A-2) Diagnose Electrical/Electronic Integrity for Series, Parallel, and Series-Parallel Circuits Using Principles of Electricity (Ohm's Law). (P-1)

Name _____ Date _____ Time on Task _____


Make/Model/Year _____ VIN _____ Evaluation: 4 3 2 1



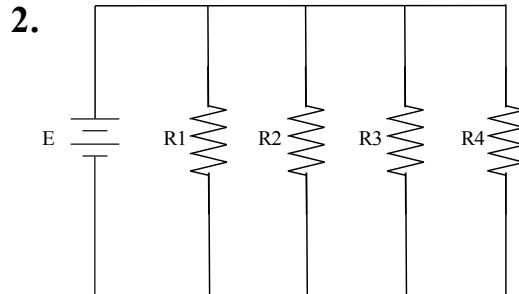
$$\begin{aligned}
 E &= 12 \text{ volts} & R1 &= 4 \text{ ohms} \\
 I_T &= \underline{\hspace{2cm}} & R2 &= 12 \text{ ohms} \\
 R1 &= 4 \text{ ohms} & R4 &= 12 \text{ ohms}
 \end{aligned}$$



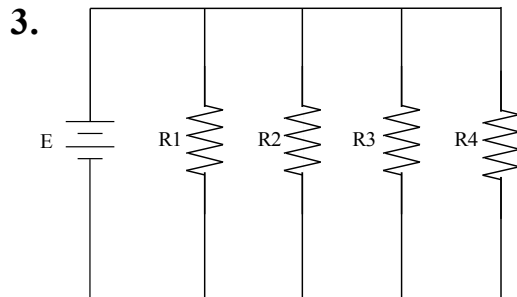
$$\begin{aligned}
 E &= \underline{\hspace{2cm}} & R1 &= 12 \text{ ohms} \\
 I_T &= 4 \text{ amperes} & R2 &= 12 \text{ ohms} \\
 R1 &= 12 \text{ ohms} & R3 &= 12 \text{ ohms}
 \end{aligned}$$



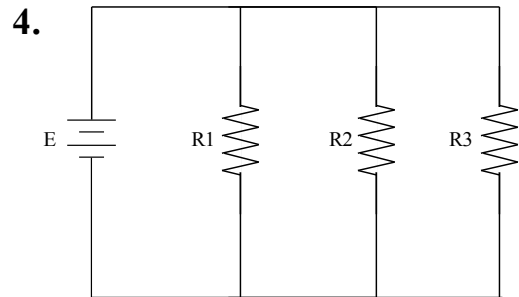
$$\begin{aligned}
 E &= \underline{\hspace{2cm}} & R2 &= 4 \text{ ohms} \\
 I_T &= 1 \text{ ampere} & R3 &= 6 \text{ ohms} \\
 R1 &= 2 \text{ ohms} & R4 &= 12 \text{ ohms}
 \end{aligned}$$


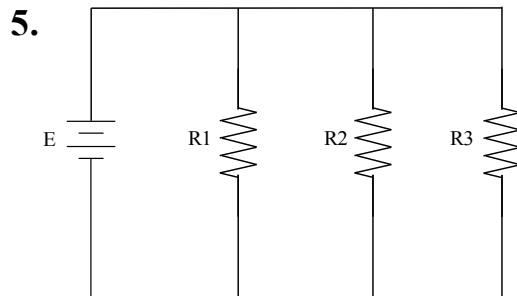
$$\begin{aligned}
 E &= 12 \text{ volts} & R2 &= 8 \text{ ohms} \\
 I_T &= \underline{\hspace{2cm}} & R3 &= 4 \text{ ohms} \\
 R1 &= 8 \text{ ohms}
 \end{aligned}$$


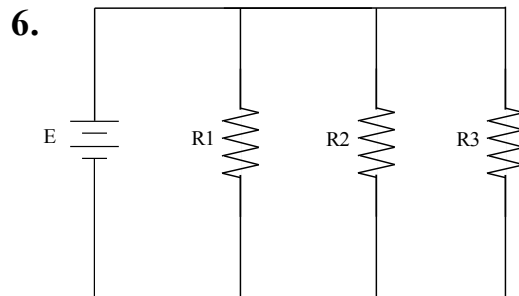
$$\begin{aligned}
 E &= 12 \text{ volts} & R2 &= 12 \text{ ohms} \\
 I_T &= 4 \text{ amperes} & R3 &= \underline{\hspace{2cm}} \\
 R1 &= 12 \text{ ohms}
 \end{aligned}$$



$$\begin{aligned}
 E &= \underline{\hspace{2cm}} & R2 &= 24 \text{ ohms} \\
 I_T &= 2 \text{ amperes} & R3 &= 12 \text{ ohms} \\
 R1 &= 24 \text{ ohms}
 \end{aligned}$$