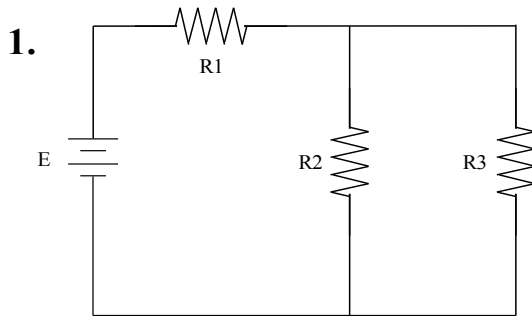


## Series-Parallel Circuit Worksheet #1


Meets NATEF Task: (A6-A-2) Diagnose Electrical/Electronic Integrity for Series, Parallel, and Series-Parallel Circuits Using Principles of Electricity (Ohm's Law). (P-1)

Name \_\_\_\_\_ Date \_\_\_\_\_ Time on Task \_\_\_\_\_


Make/Model/Year \_\_\_\_\_ VIN \_\_\_\_\_ Evaluation: 4 3 2 1



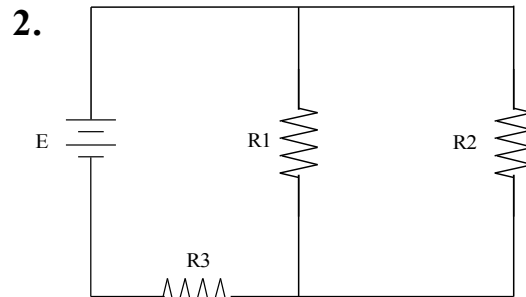
$E = 12$  volts       $R2 = 4$  ohms  
 $I_T = 3$  amperes       $R3 = 4$  ohms  
 $R1 =$  \_\_\_\_\_



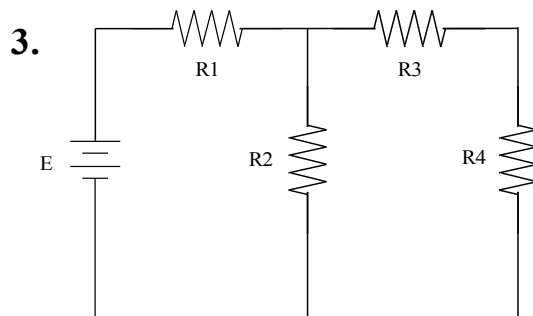
$E = 12$  volts       $R2 = 4$  ohms  
 $I_T = 3$  amperes       $R3 =$  \_\_\_\_\_  
 $R1 = 4$  ohms



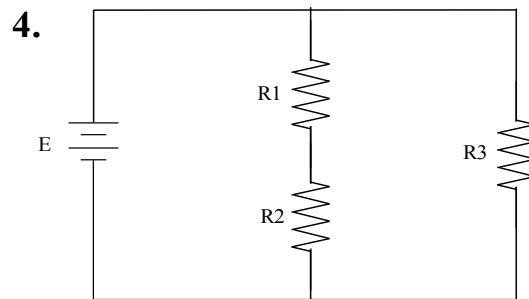
$E = 12$  volts       $R2 = 4$  ohms  
 $I_T =$  \_\_\_\_\_       $R3 = 2$  ohms  
 $R1 = 2$  ohms       $R4 = 2$  ohms



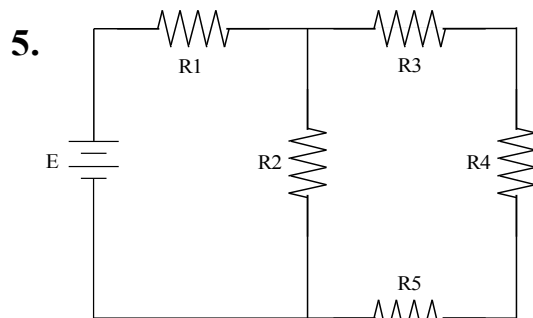$E =$  \_\_\_\_\_       $R2 = 4$  ohms  
 $I_T = 3$  amperes       $R3 = 8$  ohms  
 $R1 = 4$  ohms



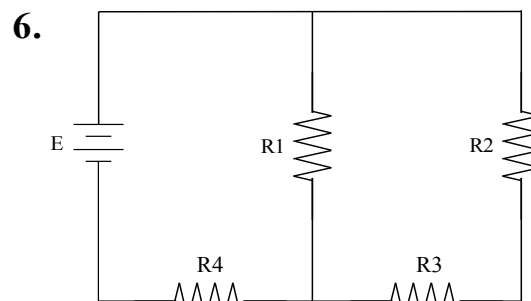$E = 12$  volts       $R3 = 2$  ohms  
 $I_T =$  \_\_\_\_\_       $R4 = 4$  ohms  
 $R1 = 2$  ohms       $R5 = 2$  ohms  
 $R2 = 8$  ohms



$E = 12$  volts       $R2 = 6$  ohms  
 $I_T =$  \_\_\_\_\_       $R3 = 6$  ohms  
 $R1 = 12$  ohms       $R4 = 2$  ohms