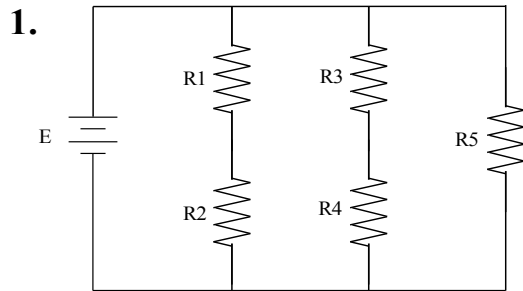


## Series-Parallel Circuit Worksheet #2


Meets NATEF Task: (A6-A-2) Diagnose Electrical/Electronic Integrity for Series, Parallel, and Series-Parallel Circuits Using Principles of Electricity (Ohm's Law). (P-1)

Name \_\_\_\_\_ Date \_\_\_\_\_ Time on Task \_\_\_\_\_


Make/Model/Year \_\_\_\_\_ VIN \_\_\_\_\_ Evaluation: 4 3 2 1



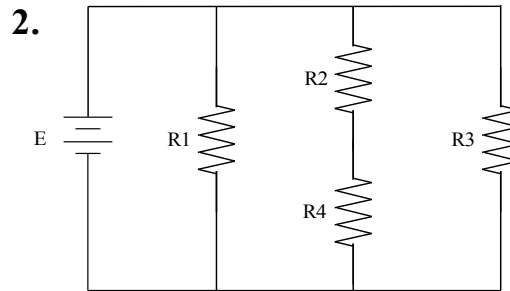
$E = 24$  volts  
 $I_T = \underline{\hspace{2cm}}$   
 $R1 = 6$  ohms  
 $R2 = 6$  ohms  
 $R3 = 6$  ohms  
 $R4 = 6$  ohms  
 $R5 = 6$  ohms



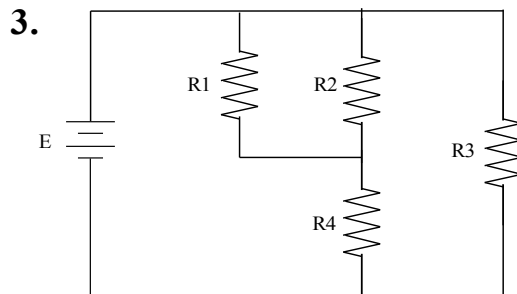
$E = \underline{\hspace{2cm}}$   
 $I_T = 12$  amperes  
 $R1 = 8$  ohms  
 $R2 = 4$  ohms  
 $R3 = 4$  ohms  
 $R4 = 4$  ohms



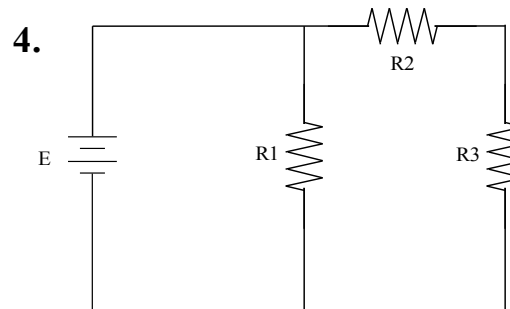
$E = 12$  volts  
 $I_T = \underline{\hspace{2cm}}$   
 $R1 = 4$  ohms  
 $R2 = 4$  ohms  
 $R3 = 4$  ohms  
 $R4 = 2$  ohms



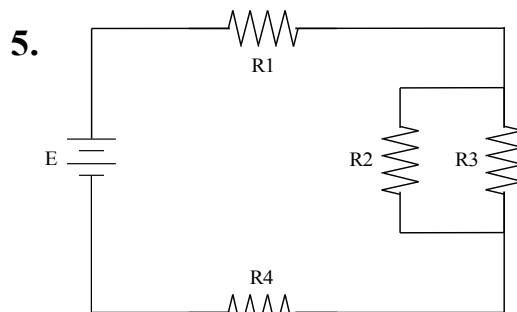$E = \underline{\hspace{2cm}}$   
 $I_T = 6$  amperes  
 $R1 = 8$  ohms  
 $R2 = 4$  ohms  
 $R3 = 4$  ohms



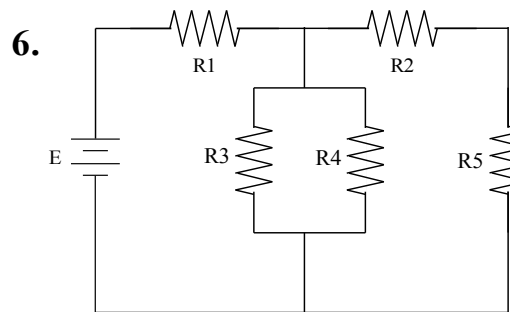$E = 12$  volts  
 $I_T = \underline{\hspace{2cm}}$   
 $R1 = 1$  ohm  
 $R2 = 2$  ohms  
 $R3 = 2$  ohms  
 $R4 = 1$  ohm



$E = 12$  volts  
 $I_T = 4$  amperes  
 $R1 = \underline{\hspace{2cm}}$   
 $R2 = 4$  ohms  
 $R3 = 4$  ohms  
 $R4 = 8$  ohms  
 $R5 = 4$  ohms