

Circuit Testing Using a Fused Jumper Wire

Meets NATEF Task: (A6-A-7) Check electrical circuits using fused jumper wire; determine the necessary action. (P-2)

Name _____ Date _____ Time on Task _____

Make/Model/Year _____ VIN _____ Evaluation: 4 3 2 1

CAUTION: A fused jumper wire should never be used to bypass an electrical load device.

- _____ 1. Check service information for a diagnostic test procedure that includes the use of a fused jumper wire.

- _____ 2. A horn circuit is a commonly used circuit to show the use of a fused jumper wire.


- a. Locate the horn (describe the location):

- b. Disconnect the wire from the horn.

- c. Connect one end of the fused jumper wire to the terminal of the horn.

- d. Touch the other end of the fused jumper wire to the positive (+) terminal of the battery.

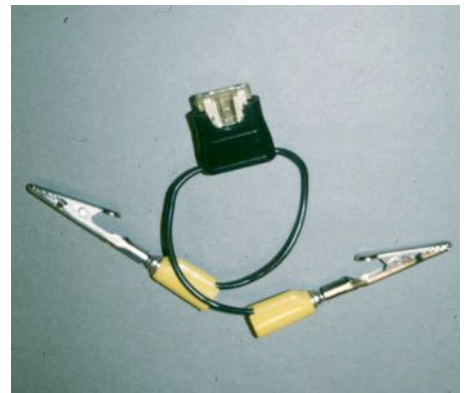- e. The horn should work. **OK** _____ **NOT OK** _____



- _____ 3. Based on the test results, what is the necessary action? _____
