

Inspect and Test Starter Switches and Connectors

Meets NATEF Task: (A6-C-5) Inspect and test switches, connectors, and wires of starter control circuit; determine necessary action. (P-2)

Name _____ Date _____ Time on Task _____

Make/Model/Year _____ VIN _____ Evaluation: 4 3 2 1

_____ 1. Check service information for the specified procedure to follow when inspecting and testing starter control circuit switches, connectors, and wires. Describe the specified procedure _____

_____ 2. Check and test all connections that are used at the starter.
 _____ Positive battery cable
 _____ Fusible link
 _____ "S" terminal wire connection
 _____ Other (describe) _____

_____ 3. What is the condition of the starter control circuit wiring? Describe any faults:

_____ 4. If any faults are found, what is the necessary action: _____

