

Test Light Usage

Meets NATEF Task: (A6-A-5) Check electrical circuits with a test light; determine the necessary action. (P-1)

Name _____ Date _____ Time on Task _____

Make/Model/Year _____ VIN _____ Evaluation: 4 3 2 1

_____ 1. Check service information regarding which wire color(s) is the brake light and which is the tail light. Using a test light, check for voltage to the brake lights and tail lights at the rear of the vehicle.

a. Brake light: ____ OK ____ NOT OK (describe fault) _____

b. Tail light: ____ OK ____ NOT OK (describe fault) _____

_____ 2. Using a test light, check all of the fuses in the vehicle.

NOTE: The ignition switch and/or lights need to be on to supply power to some fuses.

List all good fuses: _____

_____ 3. Based on the above activities, what is the necessary action? _____

