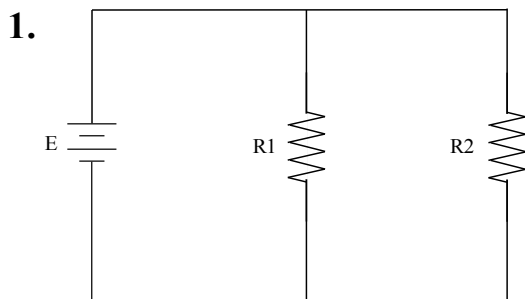


Parallel Circuit Task Sheet #1

Meets ASE Task: (A6-A-2) P-1 Diagnose Electrical/Electronic Integrity for Series, Parallel, and Series-Parallel Circuits Using Principles of Electricity (Ohm's Law).


Name _____ Date _____ Time on Task _____

Make/Model/Year _____ VIN _____ Evaluation: 4 3 2 1




$$E = 12 \text{ volts} \quad R1 = 4 \text{ ohms}$$
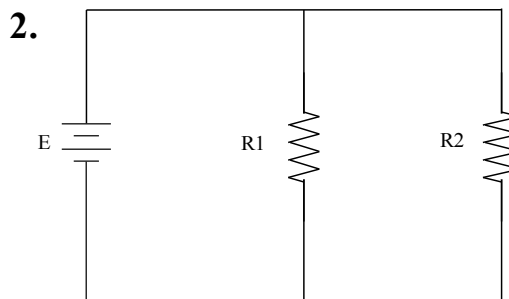
$$I_T = \underline{\hspace{2cm}} \quad R2 = 4 \text{ ohms}$$




$$E = 12 \text{ volts} \quad R1 = 6 \text{ ohms}$$
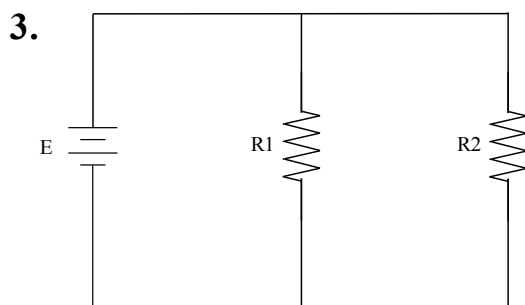
$$I_T = 4 \text{ amperes} \quad R2 = \underline{\hspace{2cm}}$$



$$E = 12 \text{ volts} \quad R1 = 12 \text{ ohms}$$

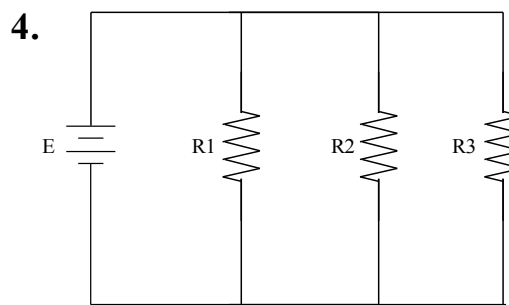
$$I_T = \underline{\hspace{2cm}} \quad R2 = 12 \text{ ohms}$$



$$E = 12 \text{ volts} \quad R2 = 4 \text{ ohms}$$

$$I_T = \underline{\hspace{2cm}} \quad R3 = 2 \text{ ohms}$$


$$R1 = 4 \text{ ohms}$$

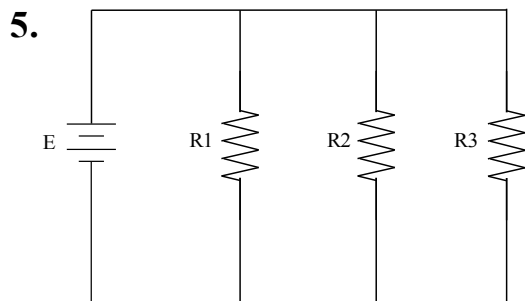

$$E = \underline{\hspace{2cm}} \quad R2 = 4 \text{ ohms}$$

$$I_T = 12 \text{ amperes} \quad R3 = 4 \text{ ohms}$$

$$R1 = 2 \text{ ohms}$$

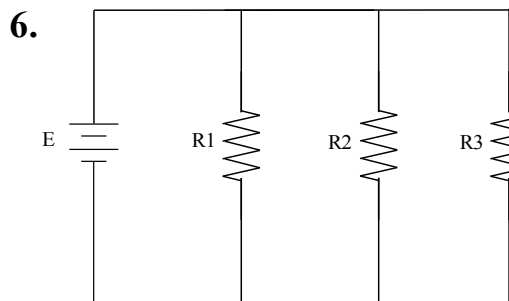

$$E = 12 \text{ volts} \quad R2 = \underline{\hspace{2cm}}$$

$$I_T = 12 \text{ amperes} \quad R3 = 2 \text{ ohms}$$

$$R1 = 4 \text{ ohms}$$