

Diagnose Electrical/Electronic Circuits

Meets ASE Task: (A6-A-7) P-1 Diagnose electrical/electronic integrity for series, parallel, and series-parallel circuits using principles of electricity (Ohm's Law).

Name _____ Date _____ Time on Task _____

Make/Model/Year _____ VIN _____ Evaluation: 4 3 2 1

_____ 1. Check service information to determine the specified diagnosis procedures to follow for a slowly operating wiper motor. This circuit is a:

- _____ Series
 _____ Parallel
 _____ Series-Parallel

_____ 2. One tail light is dim, all other exterior lighting operates normally. Check service information to determine the specified diagnostic procedure to follow for a dim tail light.

This circuit is a:

- _____ Series
 _____ Parallel
 _____ Series-Parallel

_____ 3. Check service information to determine the specified diagnostic procedure to follow to correctly diagnose a fault in a blower motor circuit.

