

Blower Motor Radio Noise

Meets ASE Task: (A7-D-1) P-1 Diagnose static and weak or no reception; determine necessary action.

Name _____ Date _____ Time on Task _____

Make/Model/Year _____ VIN _____ Evaluation: 4 3 2 1

A digital meter set to read AC volts can be used to easily check the capacitor connected to the blower motor. A blower motor generates an AC voltage as it rotates; the purpose and function of the capacitor attached to the positive power lead is to eliminate potential radio noise that could be created by the blower motor. To check to see if the capacitor is okay, follow these easy steps:

- Step 1** Set a digital multimeter to read AC volts.
- Step 2** Use a T-pin and carefully back probe the power lead at the blower motor being careful not to pierce the insulation. (The T-pin should just touch the metal terminal inside the plastic connection.)
- Step 3** Connect one lead (with AC volts, it doesn't matter which lead is connected to which terminal) to the T-pin and the other lead to a good engine or body ground.
- Step 4** Turn the blower on while observing the meter display. Check the AC voltage at all blower speeds.

Low = _____
 Medium = _____
 Medium high = _____
 High = _____

The capacitor, blower motor, and wiring are okay if the AC voltage is less than 0.5 volt (500 mV).

OK _____ NOT OK _____

What is the necessary action? _____