

# Blower Motor Circuit

**Meets ASE Task:** (A7-D-1) P-1 Diagnose operation of motor-driven accessory; determine needed action.

Name \_\_\_\_\_ Date \_\_\_\_\_ Time on Task \_\_\_\_\_

Make/Model/Year \_\_\_\_\_ VIN \_\_\_\_\_ Evaluation: 4 3 2 1

\_\_\_\_\_ 1. Check service information and determine the specified testing procedures.

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_ 2. Locate the blower motor schematic and determine the following information:

- a. Describe the location \_\_\_\_\_
- b. Is the blower motor accessible from inside the vehicle or from under the hood?

\_\_\_\_\_

c. List the wire colors and their gauge:

Power = \_\_\_\_\_


Ground = \_\_\_\_\_

\_\_\_\_\_ 3. How are the various speeds controlled?

\_\_\_\_\_ Resistor pack

\_\_\_\_\_ Electronic controller

\_\_\_\_\_ Other (describe) \_\_\_\_\_

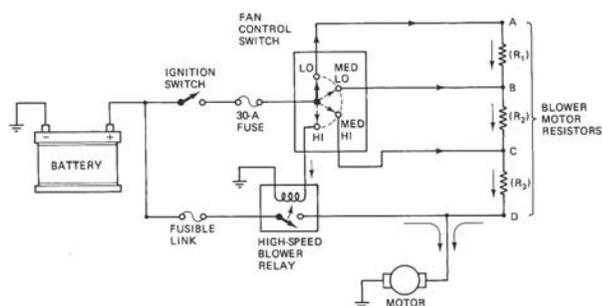

\_\_\_\_\_ 4. What fuse number (label) and amperage rating are used for the blower motor?

a. Fuse number (label) \_\_\_\_\_

b. Fuse rating \_\_\_\_\_

\_\_\_\_\_ 5. Describe the location of the ground(s) for the blower motor circuit. \_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_ 6. Measure the current draw of the blower motor on high speed.

Amperage = \_\_\_\_\_ (normal blower motor amperage draw is about 12-14 amperes)

\_\_\_\_\_ 7. Based on the inspection and test results, what is the needed action? \_\_\_\_\_

\_\_\_\_\_