



Advanced Automotive Electricity & Electronics

Chapter 2 Electrical Circuits & Ohm's Law

Opening Your Class

KEY ELEMENT	EXAMPLES
Introduce Content	This course or class covers operation and service of Advanced Automotive Electricity and Electronics Systems . It correlates material to task lists specified by ASE and NATEF.
Motivate Learners	Explain how the knowledge of how something works translates into the ability to use that knowledge to figure why the engine does not work correctly and how this saves diagnosis time, which translates into more money.
State the learning objectives for the chapter or course you are about to cover and explain this is what they should be able to do as a result of attending this session or class.	Explain the chapter learning objectives to the students. <ol style="list-style-type: none">1. Identify the parts of a complete circuit.2. Describe the characteristics of different types of circuit faults.3. Explain Ohm's law as it applies to automotive circuits.4. Explain Watt's law as it applies to automotive circuits. This chapter will help you prepare for the ASE Electrical/Electronic Systems (A6) certification test content area "A" (General Electrical/Electronic System Diagnosis).
Establish the Mood or Climate	Provide a <i>WELCOME</i> , Avoid put downs and bad jokes.
Complete Essentials	Restrooms, breaks, registration, tests, etc.
Clarify and Establish Knowledge Base	Do a round robin of the class by going around the room and having each student give their backgrounds, years of experience, family, hobbies, career goals, or anything they want to share.

ICONS

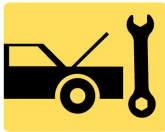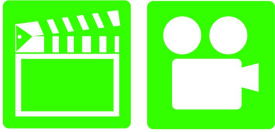

Ch02 ELECTRICAL CIRCUITS/OHM'S LAW

1. SLIDE 1 CH2 ELECTRICAL CIRCUITS/OHM'S LAW

Check for **ADDITIONAL VIDEOS & ANIMATIONS**
@ <http://www.jameshalderman.com/>
WEB SITE IS CONSTANTLY UPDATED

2. SLIDES 2-3 EXPLAIN CIRCUITS TEXT

4. **SLIDE 4 EXPLAIN** Figure 2-1 All complete circuits must have a power source, a power path, protection (fuse), an electrical load (light bulb in this case), and a return path back to the power source.








DEMONSTRATION: DEMONSTRATE BASIC ELECTRICAL CIRCUIT ON TRAINER. SHOW (FIGURE 2-1)WHAT HAPPENS WHEN CIRCUIT IS SHORTED TO GROUND

TRAINER TASK: ALLOW STUDENTS TO BLOW FUSE BY CREATING A SHORT CIRCUIT, OBSERVING WHAT IT TAKES TO CREATE SHORT CIRCUIT AND WHAT RESULTS ARE FOUND

5. **SLIDE 5 EXPLAIN** Figure 2-2 return path back to the battery can be any electrical conductor, such as a copper wire or the metal frame or body of the vehicle &
6. **SLIDE 6 EXPLAIN** Figure 2-3 electrical switch opens the circuit and no current flows. The switch could also be on the return (ground) path wire
7. **SLIDE 7 EXPLAIN** CIRCUIT FAULTS
8. **SLIDE 8 EXPLAIN** Figure 2-4 Examples of common causes of open circuits. Some of these causes are often difficult to find.
9. **SLIDE 9 EXPLAIN TECH TIP**

10. **SLIDE 10 EXPLAIN** Figure 2-5 A short circuit permits electrical current to bypass some or all of the resistance in the circuit.

11. **SLIDE 11 EXPLAIN** REAL WORLD FIX

ICONS	Ch02 ELECTRICAL CIRCUITS/OHM'S LAW
	<p>DISCUSSION: ASK STUDENTS TO DISCUSS GROUND PATH. WHY DOESN'T A SEPARATE GROUND WIRE HAVE TO BE RUN FROM THE BATTERY TO EACH ELECTRICAL LOAD? ASK STUDENTS TO DISCUSS HOW AND WHY A SHORT-TO-VOLTAGE OCCURS. WHAT IS THE REASON THAT A SHORT-TO-</p>
	<p>VOLTAGE MAY OR MAY NOT BLOW A FUSE?</p>
	<p>12. SLIDE 12 EXPLAIN CIRCUIT FAULT TYPES</p> <p>13. SLIDE 13 EXPLAIN Figure 2-6 A fuse or circuit breaker opens the circuit to prevent possible overheating damage in the event of a short circuit.</p> <p>14. SLIDE 14 EXPLAIN Figure 2-7 short-to-ground affects power side of circuit. Current flows directly to ground return, bypassing some or all of electrical loads in the circuit. There is no current in circuit past the short. A short-to ground will also cause fuse to blow.</p>
	<p>15. SLIDE 15 EXPLAIN TECH TIP</p>
	<p>16. SLIDE 16 EXPLAIN FIGURE 2-8 Electrical flow through a circuit is similar to water flowing over a waterwheel. The more the water (amperes in electricity), the greater amount of work (waterwheel). The amount of water remains constant, yet the pressure (voltage in electricity) drops as the current flows through the circuit.</p>
	<p>DISCUSSION: ASK STUDENTS TO DISCUSS EFFECTS OF HIGHER THAN-NORMAL RESISTANCE ON VARIOUS COMPONENTS IN AN AUTOMOTIVE ELECTRICAL SYSTEM. WHAT CAN CAUSE HIGH RESISTANCE?</p>
	<p>HOMEWORK: RESEARCH ON INTERNET OPPORTUNITIES FOR TECHNICIANS WHO SPECIALIZE IN ELECTRICAL SYSTEMS IN YOUR AREA. ASK THEM TO FOCUS ON FOLLOWING QUESTIONS: WHAT TYPES OF WORK ARE AVAILABLE? WHAT ARE THE TRAINING AND JOB QUALIFICATION REQUIREMENTS? WHAT IS SALARY RANGE FOR TECHNICIAN WHO IS TRAINED IN AUTOMOTIVE ELECTRICAL SYSTEMS? HAVE STUDENTS WRITE A SUMMARY OF THEIR FINDINGS AND SHARE IT WITH CLASS.</p>

ICONS

Ch02 ELECTRICAL CIRCUITS/OHM'S LAW

DEMO



QUESTION



DEMONSTRATION: USE AN INDUCTIVE AMMETER OR CHARGING SYSTEM TESTER TO SHOW THAT AMOUNT OF CURRENT LEAVING BATTERY ON POSITIVE IS RETURNED ON NEGATIVE SIDE.

17. SLIDE 17 **EXPLAIN OHM'S LAW**

Ohm's Law, Current

Ohm's Law, Resistance

Ohm's Law, Volt

18. SLIDE 18 **EXPLAIN** Figure 2-9 To calculate one unit of electricity when the other two are known, simply use your finger and cover the unit you do not know. For example, if both voltage (E) and resistance (R) are known, cover the letter I (amperes). Notice that the letter E is above the letter R, so divide the resistor's value into the voltage to determine the current in circuit electricity.

19. SLIDE 19 **EXPLAIN OHM'S LAW**

20. SLIDE 20 **EXPLAIN CHART 2.1** Ohm's law relationship with the three units of electricity.





DISCUSSION: ASK STUDENTS TO TALK ABOUT OHM'S LAW. WHAT IS APPLICATION OF OHM'S LAW IN AUTOMOTIVE WIRING CIRCUITS?

COMPLETE TASK SHEET ON ELECTRICAL CIRCUITS

STUDENTS CAN COMPLETE NATEF TASK SHEET ON OHM'S LAW: DIAGNOSE ELECTRICAL/ELECTRONIC INTEGRITY OF SERIES, PARALLEL & SERIES-PARALLEL CIRCUITS USING PRINCIPLES OF ELECTRICITY (OHM'S LAW)

21. SLIDES 21-22 **EXPLAIN WATT'S LAW**

23. SLIDE 23 **EXPLAIN** Figure 2-10 This closed circuit includes a power source, power-side wire, circuit protection (fuse), resistance (bulb), and return path wire. In this circuit, if battery has 12 volts & electrical load has 4 ohms, then current through circuit is 4 amperes.

ICONS	Ch02 ELECTRICAL CIRCUITS/OHM'S LAW
   	<p data-bbox="586 247 1406 394">DISCUSSION: ASK STUDENTS TO COMPARE OHM'S & WATT'S LAWS. WHICH LAW CAN BE USED TO DETERMINE THE DIAMETER OF WIRE NEEDED FOR A CIRCUIT?</p> <p data-bbox="586 407 927 443"><u>Math Formula, Watt</u></p> <p data-bbox="626 569 1117 604">24. SLIDE 24 EXPLAIN TECH TIP</p> <p data-bbox="626 684 1414 789">25. SLIDE 25 EXPLAIN Figure 2-11 Calculate 1 unit when other 2 are known, cover unknown unit to see what unit needs to be divided or multiplied to arrive at solution.</p> <p data-bbox="626 800 1398 1016">26. SLIDE 26 EXPLAIN Figure 2-12 “Magic circle” of most formulas for problems involving Ohm’s law. Each quarter of “pie” has formulas used to solve for a particular unknown value: current (amperes), in upper right segment; resistance (ohms), in lower right; voltage (E), in lower left; and power (watts), in upper left</p>