

# Series, Parallel, And Series-Parallel Circuits

## Chapter 3

