

# Chapter 5 Series, Parallel, And Series-Parallel Circuits

