Electrical Circuits

Meets ASE Task: Not specified by ASE

Name	Date	Time on Task	
Make/Model/Year	VIN	Evaluation: 4	3 2 1
1. Draw a complete electrical	circuit and label all of	the narts	
1. Braw a complete electrical	circuit una laber un or	the pures.	
2. What is an open circuit?			
3. Describe the difference beth	ween a short-to-voltag	e and a short-to-ground.	
-			
4. State Ohm's Law			
5. State Watt's Law			
S. State Watt 5 Daw			