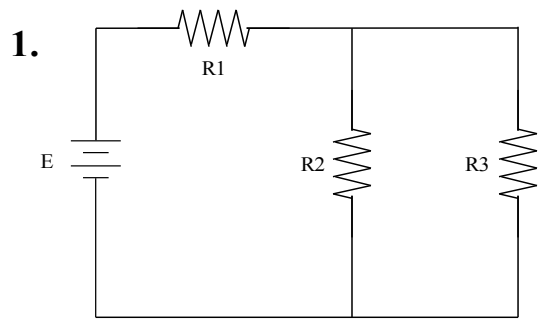


Series-Parallel Circuit Worksheet #1


Meets ASE Task: (A6-A-2) Diagnose Electrical/Electronic Integrity for Series, Parallel, and Series-Parallel Circuits Using Principles of Electricity (Ohm's Law). (P-1)

Name _____ Date _____ Time on Task _____


Make/Model/Year _____ VIN _____ Evaluation: 4 3 2 1



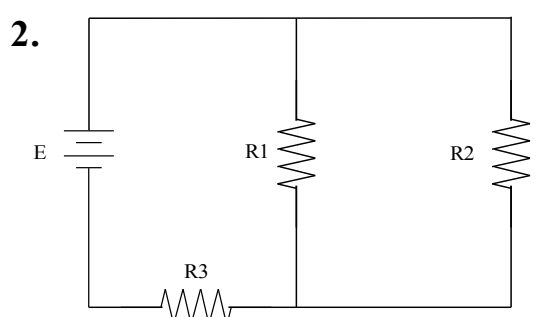
$E = 12$ volts
 $I_T = 3$ amperes
 $R1 = \underline{\hspace{2cm}}$
 $R2 = 4$ ohms
 $R3 = 4$ ohms



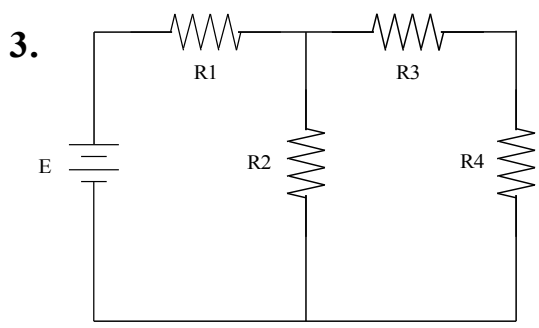
$E = 12$ volts
 $I_T = 3$ amperes
 $R1 = 4$ ohms
 $R2 = 4$ ohms
 $R3 = \underline{\hspace{2cm}}$



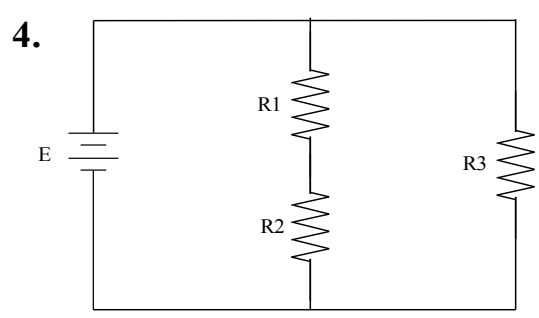
$E = 12$ volts
 $I_T = \underline{\hspace{2cm}}$
 $R1 = 2$ ohms
 $R2 = 4$ ohms
 $R3 = 2$ ohms
 $R4 = 2$ ohms



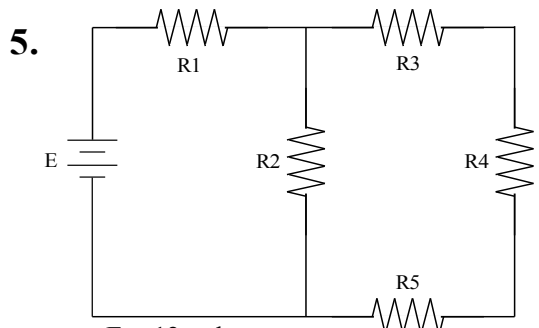$E = \underline{\hspace{2cm}}$
 $I_T = 3$ amperes
 $R1 = 4$ ohms
 $R2 = 4$ ohms
 $R3 = 8$ ohms



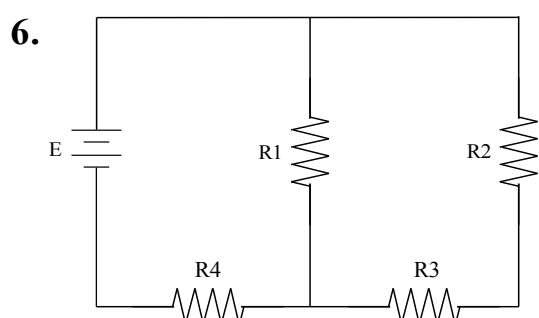$E = 12$ volts
 $I_T = \underline{\hspace{2cm}}$
 $R1 = 2$ ohms
 $R2 = 8$ ohms
 $R3 = 2$ ohms
 $R4 = 4$ ohms
 $R5 = 2$ ohms



$E = 12$ volts
 $I_T = \underline{\hspace{2cm}}$
 $R1 = 12$ ohms
 $R2 = 6$ ohms
 $R3 = 6$ ohms
 $R4 = 2$ ohms