

Online Assignment

Chapter 48

Electronic Fundamentals

Question 5

(Online) find videos about clamping diodes. (Below) list two videos that describe clamping diodes. List what a forward bias clamping diode will do to an equally positive and equally negative input sine wave or what happens with the output sine wave after going through a forward bias clamping diode. Be prepared for in-class discussion. List references.

[illegible]