

Name _____

MATCHING. Choose the item in column 2 that best matches each item in column 1.

- | | | |
|------------------------------------|-------------------------------------|-----------|
| 1) Complete path for electron flow | A) E | 1) _____ |
| 2) Caused by an open switch | B) Grounded circuit | 2) _____ |
| 3) May cause a blown fuse | C) Watts of bulb divided by voltage | 3) _____ |
| 4) Open circuit | D) Circuit | 4) _____ |
| 5) $I \times R =$ | E) Ohm's law | 5) _____ |
| 6) $E \div R =$ | F) 1000 Ω | 6) _____ |
| 7) $P = I \times E$ | G) 10,000 Ω | 7) _____ |
| 8) $E = I \times R$ | H) Short-to-voltage | 8) _____ |
| 9) Calculate amps for a bulb | I) Watt's law | 9) _____ |
| 10) 10 K Ω is the same as: | J) Watts of bulb times the voltage | 10) _____ |
| | K) No current flow | |
| | L) I | |
| | M) Open circuit | |

Answer Key

Testname: MATCH 40

1) D

Page Ref: 462

2) M

Page Ref: 463

3) B

Page Ref: 463

4) K

Page Ref: 463

5) A

Page Ref: 465

6) L

Page Ref: 465

7) I

Page Ref: 466

8) E

Page Ref:

9) C

Page Ref: 466

10) G

Page Ref: 465