
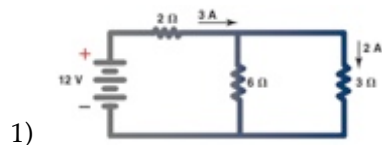


Name _____

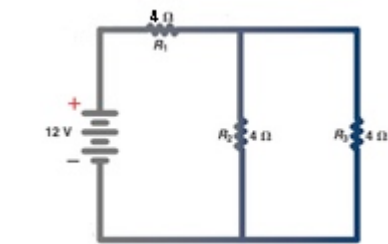MATCHING. Choose the item in column 2 that best matches each item in column 1.




2) Series-parallel circuit example



Total resistance = _____

4) Series-parallel key to calculations

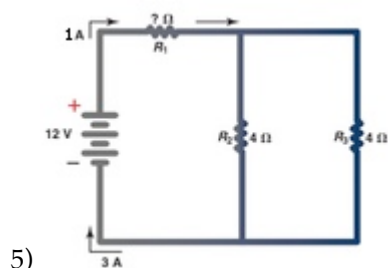

R1 = _____

A) Simplify the circuit

B) Series-parallel circuit

C) 12Ω

D) 10Ω

E) Parallel circuit

F) 6Ω

G) Dash lights

1) _____

2) _____

3) _____

4) _____

5) _____

Answer Key

Testname: AEE6_MATCH8

1) B

Page Ref: 86

2) G

Page Ref: 86

3) F

Page Ref: 87

4) A

Page Ref: 87

5) D

Page Ref: 87