

Name _____

MULTIPLE CHOICE. Choose the one alternative that best completes the statement or answers the question.

- 1) Corrosion on electrical terminals may cause _____. 1) _____
 - A) Lights to be dimmer than normal
 - B) Increased current flow in the circuit
 - C) A blown fuse after driving
 - D) None of these

- 2) High resistance in an electrical circuit can cause _____. 2) _____
 - A) Dim lights
 - B) Slow motor operation
 - C) Clicking of relays or solenoids
 - D) All of the above

- 3) The electrical path to ground may be completed by _____. 3) _____
 - A) The vehicle frame
 - B) The metal body of the vehicle
 - C) Both A and B
 - D) Neither A nor B

- 4) If the voltage increases in a circuit, what happens to the current (amperes) if the resistance remains the same? 4) _____
 - A) Increases
 - B) Decreases
 - C) Remains the same
 - D) Cannot be determined


- 5) It requires _____ volt(s) to push 1 ampere through 1 ohm of resistance. 5) _____
 - A) 1
 - B) 2
 - C) 12
 - D) 0.1

- 6) If two insulated (power side) wires were to melt together at the point where the copper conductors touched each other, the type of failure would be called a(an) _____. 6) _____
 - A) Short-to-voltage
 - B) Short-to-ground
 - C) Open
 - D) Floating ground

- 7) How many watts are consumed by a light bulb if 1.2 amperes are measured when 12 volts are applied? 7) _____
 - A) 14.4 watts
 - B) 144 watts
 - C) 10 watts
 - D) 0.10 watt

8) This circuit can be described as a(an) _____ circuit.

8) _____

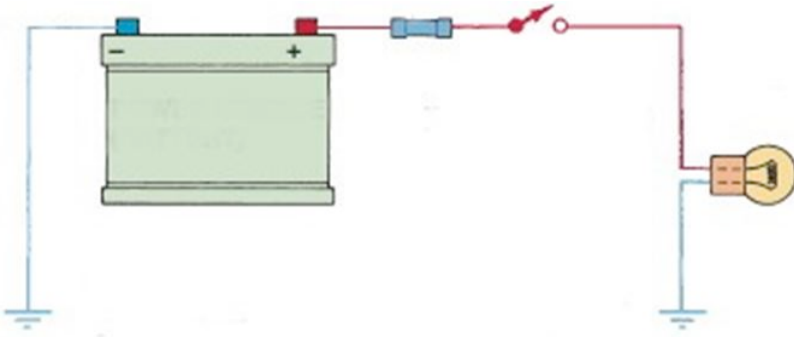

- A) Short
- B) Long
- C) Closed
- D) Open

9) Conductors that become too hot _____.

9) _____

- A) Create excessive resistance
- B) Could be the result of a short to ground before the load
- C) Both A and B
- D) Neither A nor B

10) A circuit with excessive current flow _____.

10) _____

- A) May create excess heat in conductors
- B) May cause a fuse to blow
- C) Both A and B
- D) Neither A nor B

Answer Key

Testname: AEE6_5B

1) A

Page Ref: 66-69

2) D

Page Ref: 66

3) C

Page Ref: 64

4) A

Page Ref: 67-68

5) A

Page Ref: 61

6) A

Page Ref: 65-66

7) A

Page Ref: 69

8) D

Page Ref: 65-66

9) C

Page Ref: 65-66

10) C

Page Ref: 65-66