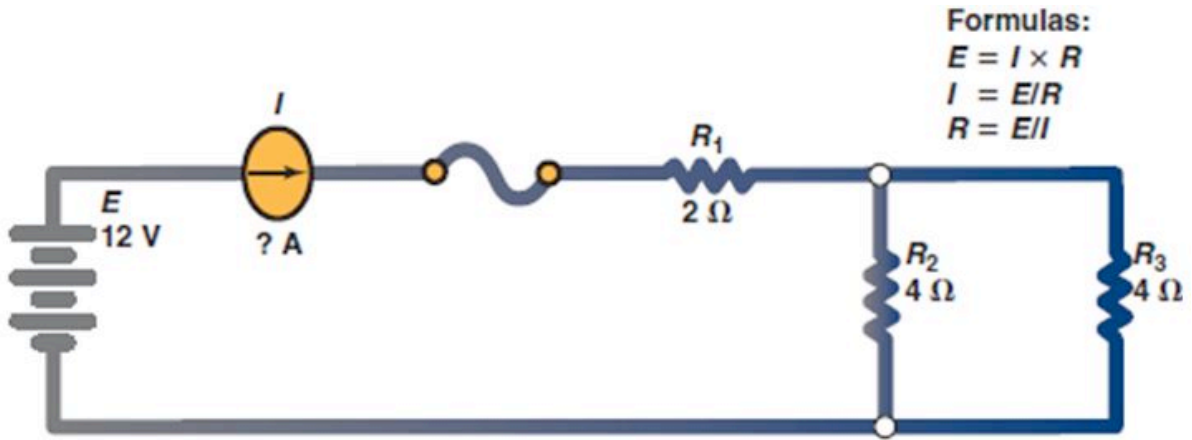


Name _____

MULTIPLE CHOICE. Choose the one alternative that best completes the statement or answers the question.

1) See **Figure 8-8** to solve for total resistance (R_T) and total current (I).

1) _____




$E = 12 \text{ V}$
 $R_1 = 2 \Omega$
 $R_2 = 4 \Omega$
 $R_3 = 4 \Omega$
 $R_T = 4 \Omega$
 $I =$

- A) 10 ohms, 1.2 A
- B) 4 ohms, 3 A
- C) 6 ohms, 2 A
- D) 2 ohms, 6 A

2) See **Figure 8-11** to solve for R_1 and total resistance (R_T).

2) _____

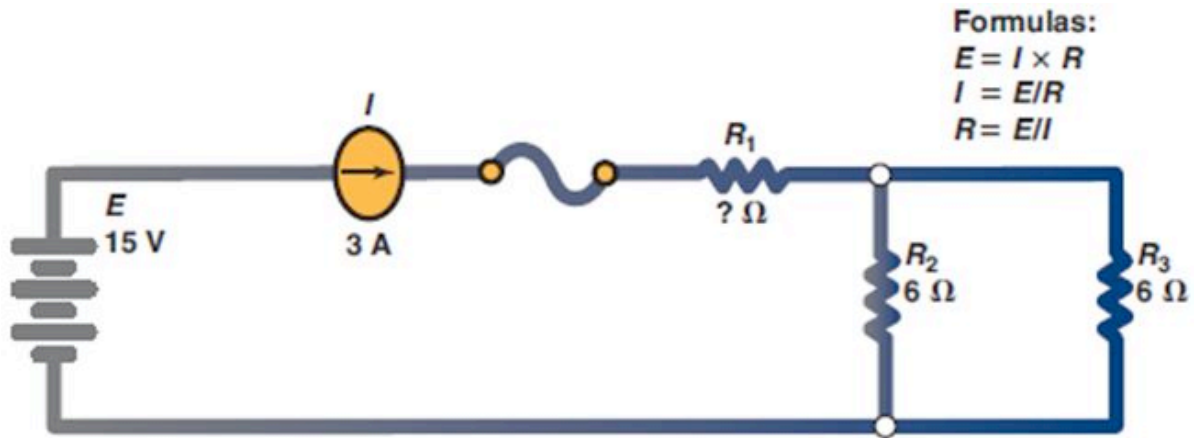


$E = 15 \text{ V}$
 $R_1 =$
 $R_2 = 6 \Omega$
 $R_3 = 6 \Omega$
 $R_T =$
 $I = 3 \text{ A}$

- A) 3 ohms; 15 ohms
- B) 1 ohm; 15 ohms
- C) 2 ohms; 5 ohms
- D) 5 ohms; 5 ohms

3) Calculate the total resistance (R_T) for the circuit in the figure below and determine the total current (I_t).

3) _____

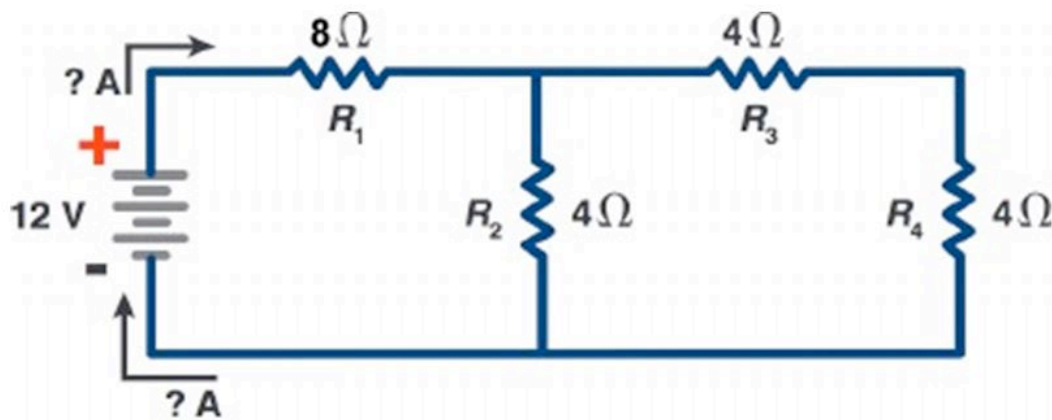

- A) 1 A
- B) 2 A
- C) 6 A
- D) 10 A


4) Which of the following is true regarding series-parallel circuits? 4) _____

A) Voltages are always equal across each load divided by the source voltage in the branches.
 B) Current is equal throughout the circuit.
 C) Only one current path is possible.
 D) Source voltage minus any voltage drop across loads wired in series is the parallel voltage.

5) Half of the dash is dark. Technician A says that a defective dash light dimmer could be the cause, because it is in series with the bulbs that are in parallel. Technician B says that one or more bulbs could be defective. Which technician is correct? 5) _____

A) Technician A only
 B) Technician B only
 C) Both technicians
 D) Neither technician

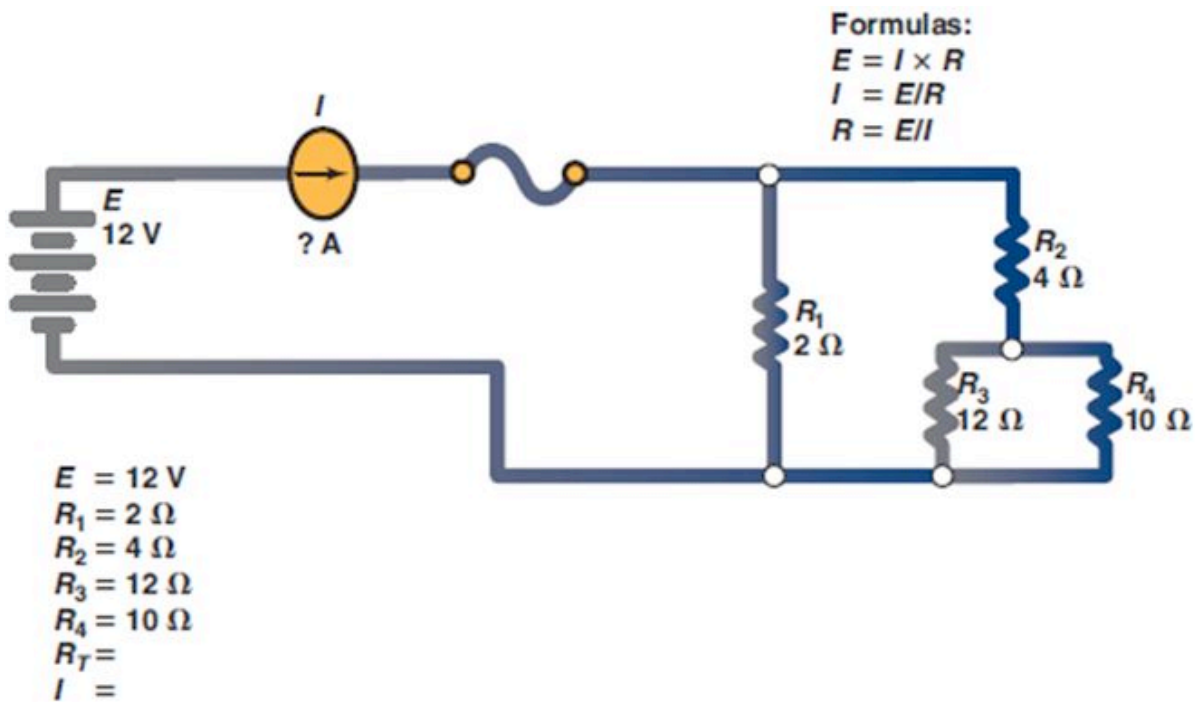
6) See Figure 8-14 to solve for total resistance (R_T) and total current (I_t). 6) _____



- A) 1.5 ohms; 8 amperes
 B) 18 ohms; 0.66 amperes
 C) 6 ohms; 2 amperes
 D) 5.5 ohms; 2.2 amperes

7) See **Figure 8-13** to solve for the value of E and total resistance (R_T).

7) _____

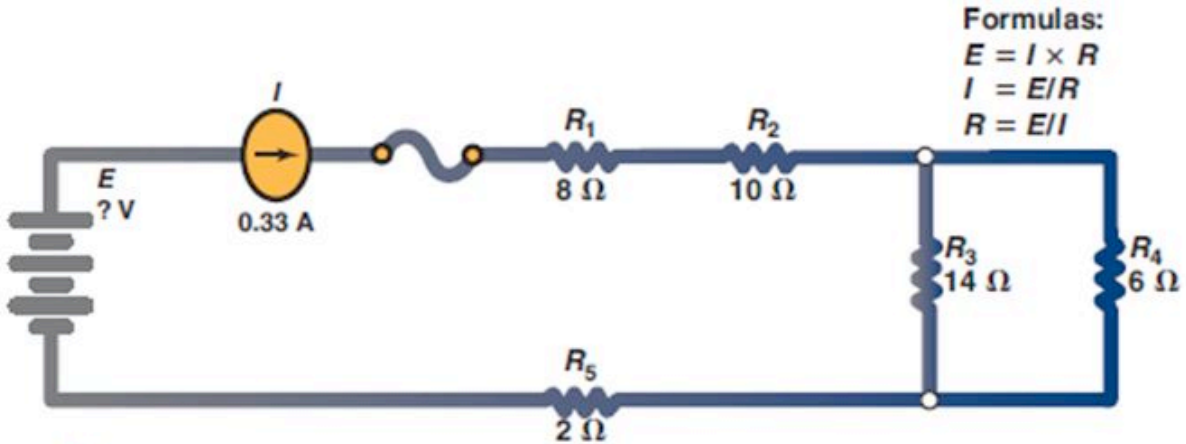


- $E =$
- $R_1 = 8 \Omega$
- $R_2 = 10 \Omega$
- $R_3 = 14 \Omega$
- $R_4 = 6 \Omega$
- $R_5 = 2 \Omega$
- $R_T =$
- $I = 0.33 \text{ A}$

- A) 13.2 volts; 40 ohms
- B) 11.2 volts; 34 ohms
- C) 8 volts; 24.2 ohms
- D) 8.6 volts; 26 ohms

8) Calculate the current flow in this circuit. (Round off to 2 decimal points.)


8) _____

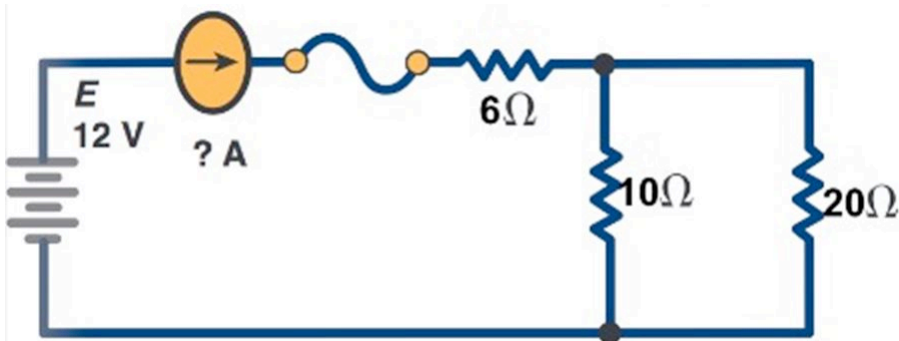

- A) About 0.95 amps
- B) About 0.33 amps
- C) About 3 amps
- D) About 1.05 amps

9) See **Figure 8-10** to solve for voltage (E) and total resistance (R_T).

9) _____

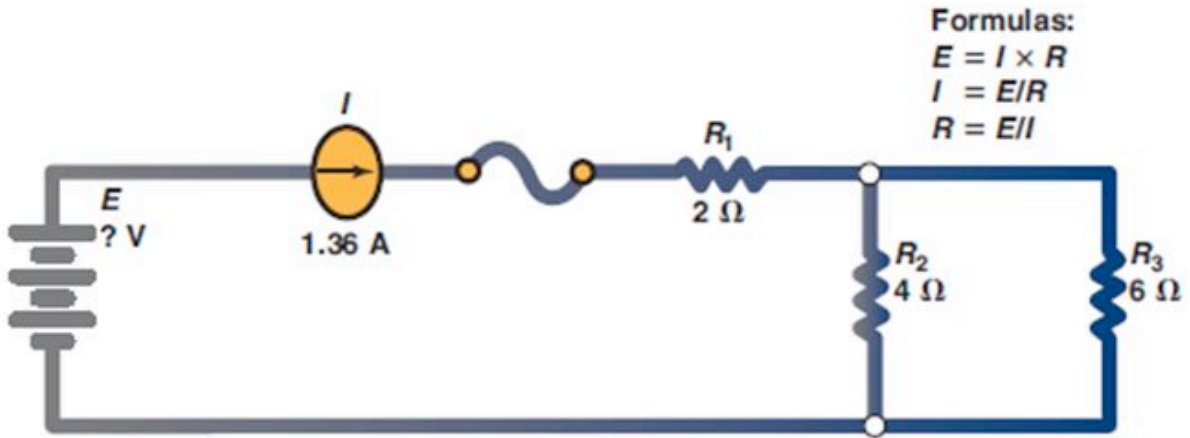


$E =$
 $R_1 = 2 \Omega$
 $R_2 = 4 \Omega$
 $R_3 = 6 \Omega$
 $R_T =$
 $I = 1.36 \text{ A}$

- A) 16.3 volts; 12 ohms
- B) 3.3 volts; 2.4 ohms
- C) 1.36 volts; 1 ohm
- D) 6 volts; 4.4 ohms

10) Determine the unknown resistor value in the figure below and determine the value of R_1 .

10) _____

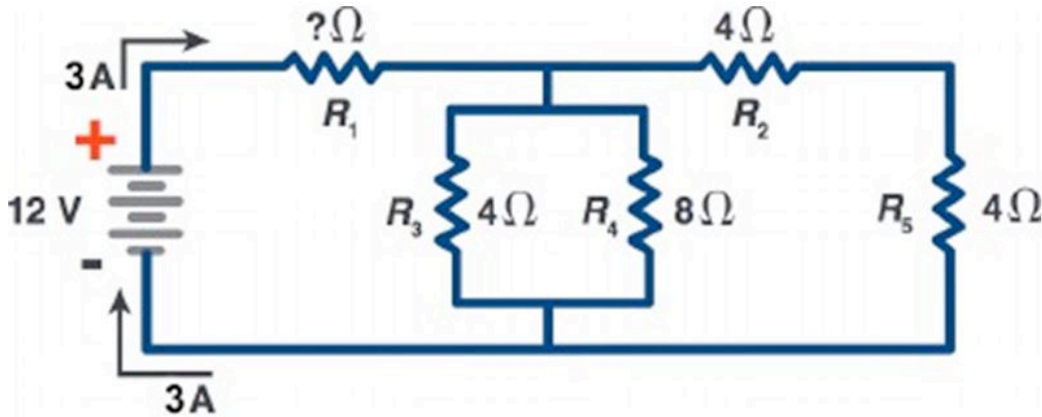

- A) 1 Ω
- B) 2 Ω
- C) 3 Ω
- D) 4 Ω

Answer Key

Testname: AEE6_8A

1) B

Page Ref: 87-88

2) C

Page Ref: 87-88

3) A

Page Ref: 87-88

4) D

Page Ref: 96-87

5) B

Page Ref: 86-87

6) A

Page Ref: 87-88

7) C

Page Ref: 87-88

8) A

Page Ref: 87-88

9) D

Page Ref: 87-88

10) B

Page Ref: 87-88