

Name _____

SHORT ANSWER. Write the word or phrase that best completes each statement or answers the question.

1) How should two capacitors be electrically connected if greater capacitance is needed?

2) Why is a large capacitor used in some high-powered sound systems?

3) How does a capacitor store an electrical charge?

4) How can a capacitor be used as a power source?

5) How can a capacitor be used as a noise filter?

Answer Key

Testname: AEE6_SHORT13

- 1) To increase the capacitance, two capacitors should be connected in parallel.
Page Ref: 156
- 2) A capacitor can be used to supply electrical power for short bursts in an audio system to help drive the speakers. Woofers and subwoofers require a lot of electrical current that often cannot be delivered by the amplifier itself.
Page Ref: 155
- 3) A capacitor stores an electrical charge by using a condenser, such as aluminum foil separated by an insulator, where electrons are stored at a voltage potential.
Page Ref: 153
- 4) A capacitor can be used as a power source if it is first charged by being connected to an electrical circuit. When the circuit is opened, the capacitor can supply electrical current when it is discharged through a circuit.
Page Ref: 155
- 5) A capacitor is used on a noise filter because most radio noise is AC and a capacitor passes AC voltage. A capacitor connected to the power lead will then pass the AC voltage to ground through the capacitor without affecting the DC power line.
Page Ref: 155