

Name _____

MATCHING. Choose the item in column 2 that best matches each item in column 1.

- | | | |
|--|---------------------------|----------|
| 1) Resistances add together for total resistance | A) Lowers resistance | 1) _____ |
| 2) Series circuit current | B) Decreases current | 2) _____ |
| 3) Current adds together for total current | C) Parallel circuit | 3) _____ |
| 4) More loads in a series circuit | D) Ohmmeter test | 4) _____ |
| 5) More loads in parallel | E) Voltage drop test | 5) _____ |
| 6) Loads in parallel | F) Series circuit | 6) _____ |
| 7) A dynamic test for resistance | G) The same at all points | 7) _____ |
| 8) Loads in series | H) Increases resistance | 8) _____ |
| | I) Increases current | |

Answer Key

Testname: AEEP8_MATCH5

1) F

Page Ref: 74

2) G

Page Ref: 74

3) C

Page Ref: 76

4) B

Page Ref: 73

5) I

Page Ref: 76

6) A

Page Ref: 76

7) E

Page Ref: 74

8) H

Page Ref: 74