Name			

PLE CHOICE. Choose the one alternative that best completes the statement or answers the quest	uon.
1) What controls the operation of a pulse-wiper system?	1)
A) A resistor that controls current flow to the wiper motor	
B) A solid-state (electronic) module	
C) A variable speed gem set	
D) A transistor	
2) The horn switch on the steering wheel of a vehicle that uses a horn relay	2)
A) sends electrical power to the horns	
B) provides the ground circuit for the horn	
C) grounds the control side of the relay	
D) provides power (12 V) to the horn relay	
3) To determine if a windshield wiper problem is electrical or mechanical, the technician should .	3)
A) Disconnect the linkage from the windshield wiper motor and operate the windshield wiper	
B) Check to see if the fuse is blown	
C) Check the condition of the wiper blades	
D) Check the washer fluid for contamination	
4) Power seats use a(n) to move the seats.	4)
A) lever	,
B) large solenoid	
C) PM electric motor	
D) springs	
5) How is the panel of a sunroof opened and closed?	5)
A) With a reversible PM motor	
B) By way of vacuum actuators	
C) With a handle and cables	
D) None of these	
6) Remote start systems include what restriction that could prevent the engine from being started?	6)
A) The remote is inside the vehicle	
B) The distance away from the vehicle exceeds the range of the transmitter	
C) The doors are not locked	
D) Any of these	
7) All of these could cause the wiper motor to run but NOT move the wipers, EXCEPT	
A) stripped gears in the gearbox	
B) loose or separated motor-to-gearbox connection	
C) loose linkage to the motor connection	
D) poor ground connection at the wiper switch	

8) When checking the operation of a rear window defogger with a voltmeter,	8)	
A) the voltmeter should be set to read AC volts		
B) the voltmeter should read close to battery voltage anywhere on the grid		
C) voltage should be available anytime at the power side of the grid because the control circuit just completes the ground side of the grid circuit		
D) the voltmeter should indicate decreasing voltage when the grid is tested across the width of the glass		
9) In most recent model vehicles, the horn button is an input to the, which then activates	9)	
the horn circuit.		
A) horn relay		
B) instrument cluster		
C) BCM		
D) fuse controller		
10) A bidirectional scan tool allows the technician to run the wiper motor forward and backwards.		
A) True		
B) False		

Answer Key

Testname: AEEP8_23B

- 1) B
 - Page Ref: 355
- 2) C
 - Page Ref: 353
- 3) A
 - Page Ref: 356
- 4) C
 - Page Ref: 371
- 5) A
 - Page Ref: 370
- 6) D
 - Page Ref: 379
- 7) D
 - Page Ref: 356
- 8) D
 - Page Ref: 365
- 9) C
 - Page Ref: 353
- 10) B
 - Page Ref: 356