

Name _____

MULTIPLE CHOICE. Choose the one alternative that best completes the statement or answers the question.

- 1) In a series circuit with two resistors, the resistor with the highest resistance will drop _____ volts than the lowest resistance. 1) _____
 - A) more
 - B) less
 - C) the same
 - D) None of these

- 2) If one branch of a parallel circuit loses continuity, the other branches will still each receive source voltage and ground. 2) _____
 - A) True
 - B) False

- 3) Technician A says that the sum of the voltage drops in a series circuit should equal the source voltage. Technician B says the current (amperes) varies depending on the value of the resistance in a series circuit. Which technician is correct? 3) _____
 - A) Technician A only
 - B) Technician B only
 - C) Both technicians A and B
 - D) Neither technician A nor B

- 4) As additional branches are added to a parallel circuit, total circuit amperage _____. 4) _____
 - A) increases
 - B) decreases
 - C) remains the same
 - D) None of these

- 5) In a series circuit _____. 5) _____
 - A) total circuit resistance is equal to the sum of all resistances in the circuit
 - B) current flow is constant at any point in the circuit
 - C) Both A and B
 - D) Neither A nor B

- 6) Knowledge of parallel circuit fundamentals is necessary to diagnose _____. 6) _____
 - A) port fuel injection circuits
 - B) diesel glow plug circuits
 - C) add-on lighting circuits
 - D) All of these

- 7) If a 12-volt battery is connected to a series circuit with three resistors of 2 ohms, 4 ohms, and 6 ohms, how much current will flow through the circuit? 7) _____
 - A) 1 amp
 - B) 2 amp
 - C) 3 amp
 - D) 4 amp

8) The total circuit resistance of a parallel circuit is always _____ the lowest resistance present in any branch of the circuit. 8) _____

- A) less than
- B) more than
- C) equal to
- D) None of these

9) The amperage in a series circuit is _____. 9) _____

- A) the same anywhere in the circuit
- B) varies in the circuit due to the different resistances
- C) high at the beginning of the circuit and decreases as the current flows through the resistance
- D) always less returning than leaving the battery

10) The sum of currents in each branch of a parallel circuit will _____ total circuit current. 10) _____

- A) equal
- B) be more than
- C) be less than
- D) None of these

Answer Key

Testname: AEEP8_5B

1) A

Page Ref: 73

2) A

Page Ref: 76

3) C

Page Ref: 73

4) A

Page Ref: 76

5) C

Page Ref: 74

6) D

Page Ref: 77

7) A

Page Ref: 73

8) A

Page Ref: 76

9) A

Page Ref: 74

10) A

Page Ref: 76