

Name _____

MATCHING. Choose the item in column 2 that best matches each item in column 1.

- | | | |
|--|---------------------------|----------|
| 1) Resistances add together for total resistance | A) Increases current | 1) _____ |
| 2) Series circuit current | B) Lowers resistance | 2) _____ |
| 3) Current adds together for total current | C) Series circuit | 3) _____ |
| 4) More loads in a series circuit | D) Parallel circuit | 4) _____ |
| 5) More loads in parallel | E) Decreases current | 5) _____ |
| 6) Loads in parallel | F) Increases resistance | 6) _____ |
| 7) A dynamic test for resistance | G) Ohmmeter test | 7) _____ |
| 8) Loads in series | H) Voltage drop test | 8) _____ |
| | I) The same at all points | |

Answer Key

Testname: AAEE_MATCH3

1) C

Page Ref: 18

2) I

Page Ref: 18

3) D

Page Ref: 22

4) E

Page Ref: 18

5) A

Page Ref: 22

6) B

Page Ref: 22

7) H

Page Ref: 20

8) F

Page Ref: 18