

Name _____

MULTIPLE CHOICE. Choose the one alternative that best completes the statement or answers the question.

- 1) Which of these tools is MOST likely to be used to determine the starter circuit voltage drop test? 1) _____
 - A) Meg ohmmeter
 - B) Voltmeter
 - C) Ohmmeter
 - D) Ammeter


- 2) A vehicle equipped with a V-8 engine does not crank fast enough to start. Technician A says that the battery could be discharged or defective. Technician B says that the negative cable could be loose at the battery. Who is right? 2) _____
 - A) A only
 - B) B only
 - C) Both A and B
 - D) Neither A nor B

- 3) A cranking system voltage drop test is being done. Technician A says that the higher the voltage drop, the lower the resistance in the circuit. Technician B says that a high voltage drop in the cranking circuit wiring can cause slow engine cranking. Who is right? 3) _____
 - A) A only
 - B) B only
 - C) Both A and B
 - D) Neither A nor B

- 4) Bench testing of a starter should be done _____. 4) _____
 - A) After reassembling an old starter
 - B) Before installing a new starter
 - C) After removing the old starter
 - D) Both A and B

- 5) A technician connects one lead of a digital voltmeter to the positive (+) terminal of the battery and the other meter lead to the battery terminal (B) of the starter solenoid and then cranks the engine. During cranking, the voltmeter displays a reading of 878 mV. Technician A says that this reading indicates that the resistance of the positive battery cable is too high. Technician B says that this reading indicates that the starter is defective. Who is right? 5) _____
 - A) A only
 - B) B only
 - C) Both A and B
 - D) Neither A nor B

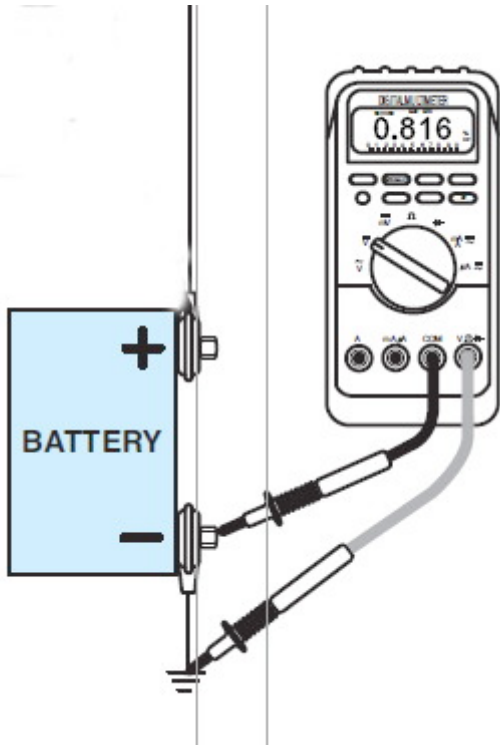6) This voltage reading was obtained while cranking the engine. The indicated reading (0.816 V) is 6) _____



- A) Too high
- B) Too low
- C) An inconclusive measurement
- D) Incorrectly done

7) Slow cranking by the starter can be caused by all of these, EXCEPT _____. 7) _____

- A) A low or discharged battery
- B) Corroded or dirty battery cables
- C) Engine mechanical problems
- D) Open neutral safety switch

8) With the armature removed from the starter motor, the field coils should be tested for opens and grounds using which of these tools? 8) _____

- A) Powered test light
- B) Ohmmeter
- C) Ammeter
- D) Either A or B

9) All of these can cause a starter not to rotate, EXCEPT _____. 9) _____

- A) Defective starter drive
- B) Shorted field coils
- C) Defective armature
- D) Seized engine crankshaft

- 10) Technician A says that the cranking circuit should be tested for proper amperage draw.
Technician B says that an open in the control circuit will not prevent starter motor operation.
Who is right?
- A) A only
 - B) B only
 - C) Both A and B
 - D) Neither A nor B

10) _____

Answer Key

Testname: AAEE_10A

1) B

Page Ref: 117

2) C

Page Ref: 123

3) B

Page Ref: 117

4) D

Page Ref: 122

5) A

Page Ref: 117

6) A

Page Ref: 117

7) D

Page Ref: 123

8) D

Page Ref: 121

9) A

Page Ref: 123

10) A

Page Ref: 117-119