

Name _____

MULTIPLE CHOICE. Choose the one alternative that best completes the statement or answers the question.

- 1) In an incomplete circuit _____. 1) _____
 - A) No current will flow
 - B) No voltage is present
 - C) Both A and B
 - D) Neither A nor B

- 2) How many watts are consumed by a light bulb if 1.2 amperes are measured when 12 volts are applied? 2) _____
 - A) 14.4 watts
 - B) 144 watts
 - C) 10 watts
 - D) 0.10 watt

- 3) A loose ground connection _____. 3) _____
 - A) Causes reduced current flow
 - B) Causes less power to be available to the electrical components
 - C) Both A and B
 - D) Neither A nor B

- 4) High resistance in a circuit can cause _____. 4) _____
 - A) Dim lights
 - B) Slow motor operation
 - C) Clicking of relays or solenoids
 - D) Any of the above

- 5) In a 12 volt circuit with 2000 ohms of resistance, how much current will flow? 5) _____
 - A) .006 A
 - B) 166 A
 - C) There will be no current flow
 - D) 120 A

- 6) In a 12 volt circuit with a resistance of 12 ohms, how much current will flow? 6) _____
 - A) 12 A
 - B) 1 A
 - C) 0.1 A
 - D) 10 A

- 7) If the voltage increases in a circuit, what happens to the current (amperes) if the resistance stays the same? 7) _____
 - A) Increases
 - B) Decreases
 - C) Remains the same
 - D) Cannot be determined

- 8) If 200 amperes flow from the positive terminal of a battery and operate the starter motor, how many amperes will flow back to the negative terminal of the battery? 8) _____
- A) 200 amperes
 - B) Zero
 - C) About one-half (100 amperes)
 - D) Cannot be determined
- 9) It requires _____ volt(s) to push 1 ampere through 1 ohm of resistance. 9) _____
- A) 1
 - B) 2
 - C) 12
 - D) None of these
- 10) A complete circuit that is continuous from source through loads and back to ground has _____ 10) _____
- A) Continuity
 - B) Congruency
 - C) Both A and B
 - D) Neither A nor B

Answer Key

Testname: AAEE_2A

1) A

Page Ref: 12

2) A

Page Ref: 15

3) C

Page Ref: 13

4) D

Page Ref: 13

5) A

Page Ref: 15

6) A

Page Ref: 15

7) A

Page Ref: 15

8) A

Page Ref: 14

9) A

Page Ref: 14

10) A

Page Ref: 11