

Chapter 5

Series, Parallel, And Series-Parallel Circuits

