


Use Wiring Diagrams During Diagnosis

Meets ASE Task: (A6-A-9) P-1 Use wiring diagrams during the diagnosis of electrical/electronic circuit problems.

Name _____ Date _____ Time on Task _____

Make/Model/Year _____ VIN _____ Evaluation: 4 3 2 1

1. Examine the following wiring diagram.

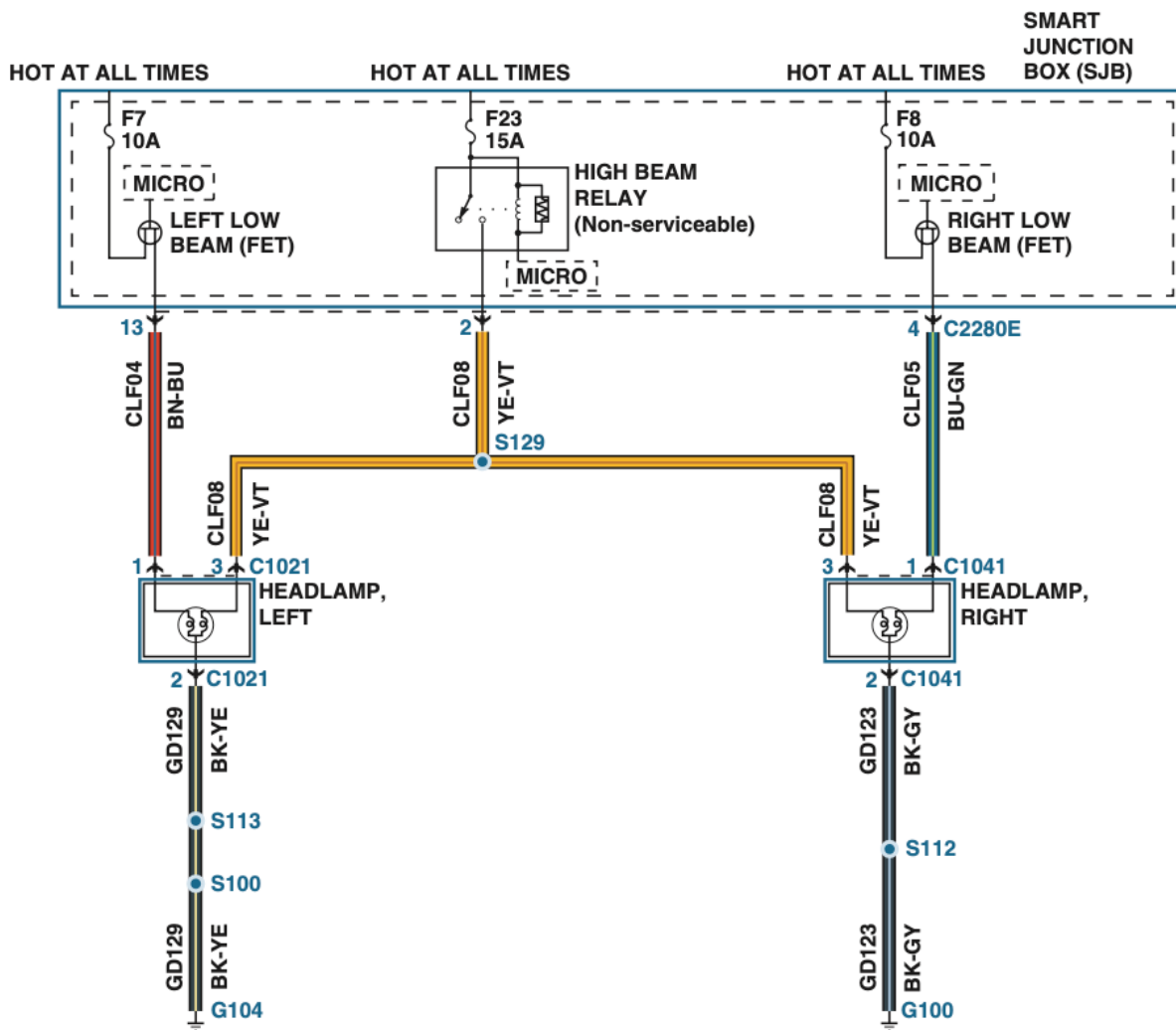

2. The vehicle problem is that the left headlamp does not light on high or low beam. The right headlamp lights normally. Use the diagram to identify where the fault could be.
