

Name \_\_\_\_\_

**MATCHING. Choose the item in column 2 that best matches each item in column 1.**

- |                                    |                                     |           |
|------------------------------------|-------------------------------------|-----------|
| 1) Complete path for electron flow | A) E                                | 1) _____  |
| 2) Caused by an open switch        | B) Grounded circuit                 | 2) _____  |
| 3) May cause a blown fuse          | C) Watts of bulb divided by voltage | 3) _____  |
| 4) Open circuit                    | D) Circuit                          | 4) _____  |
| 5) $I \times R =$                  | E) Ohm's law                        | 5) _____  |
| 6) $E \div R =$                    | F) 1000 $\Omega$                    | 6) _____  |
| 7) $P = I \times E$                | G) 10,000 $\Omega$                  | 7) _____  |
| 8) $E = I \times R$                | H) Short-to-voltage                 | 8) _____  |
| 9) Calculate amps for a bulb       | I) Watt's law                       | 9) _____  |
| 10) 10 K $\Omega$ is the same as:  | J) Watts of bulb times the voltage  | 10) _____ |
|                                    | K) No current flow                  |           |
|                                    | L) I                                |           |
|                                    | M) Open circuit                     |           |

## Answer Key

Testname: MATCH 40

1) D

Page Ref: 462

2) M

Page Ref: 463

3) B

Page Ref: 463

4) K

Page Ref: 463

5) A

Page Ref: 465

6) L

Page Ref: 465

7) I

Page Ref: 466

8) E

Page Ref:

9) C

Page Ref: 466

10) G

Page Ref: 465