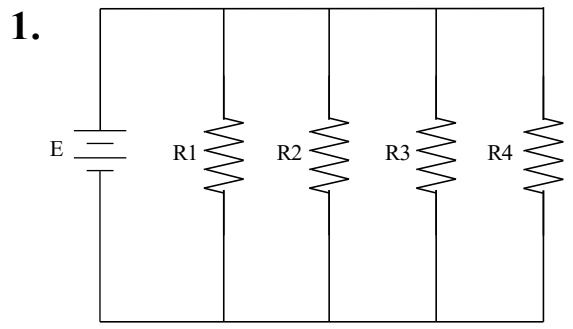


Parallel Circuit Worksheet #2


Meets ASE Task: (A6-A-2) P-1 Diagnose electrical/electronic integrity for series, parallel, and series-parallel circuits using principles of electricity (Ohm's Law).

Name _____ Date _____ Time on Task _____


Make/Model/Year _____ VIN _____ Evaluation: 4 3 2 1



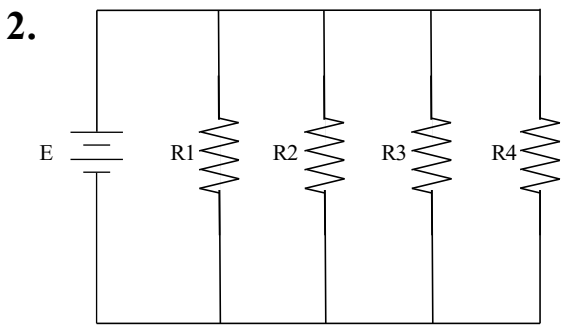
$E = 12 \text{ volts}$ $R2 = 4 \text{ ohms}$
 $I_T = \underline{\hspace{2cm}}$ $R3 = 12 \text{ ohms}$
 $R1 = 4 \text{ ohms}$ $R4 = 12 \text{ ohms}$



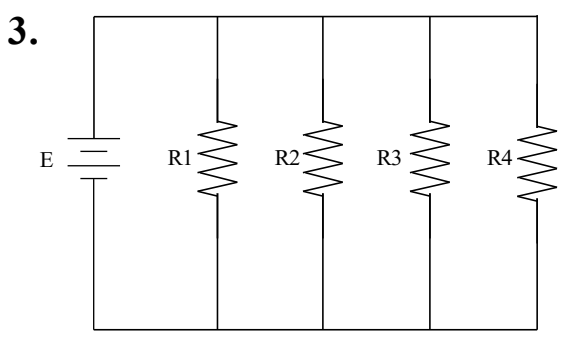
$E = \underline{\hspace{2cm}}$ $R2 = 12 \text{ ohms}$
 $I_T = 4 \text{ amperes}$ $R3 = 12 \text{ ohms}$
 $R1 = 12 \text{ ohms}$ $R4 = 12 \text{ ohms}$



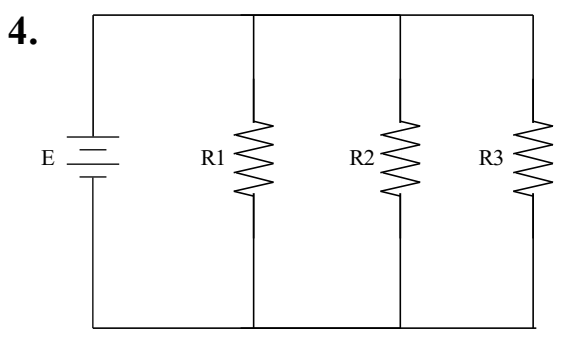
$E = \underline{\hspace{2cm}}$ $R2 = 4 \text{ ohms}$
 $I_T = 1 \text{ ampere}$ $R3 = 6 \text{ ohms}$
 $R1 = 2 \text{ ohms}$ $R4 = 12 \text{ ohms}$



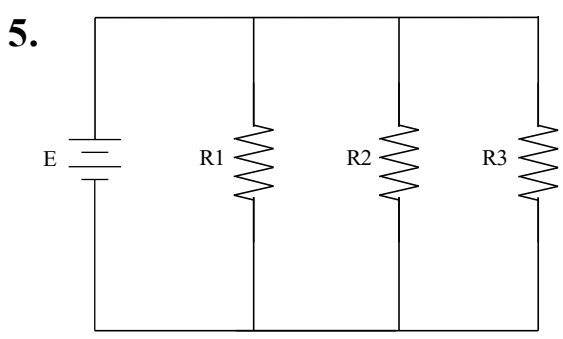$E = 12 \text{ volts}$ $R2 = 8 \text{ ohms}$
 $I_T = \underline{\hspace{2cm}}$ $R3 = 4 \text{ ohms}$
 $R1 = 8 \text{ ohms}$



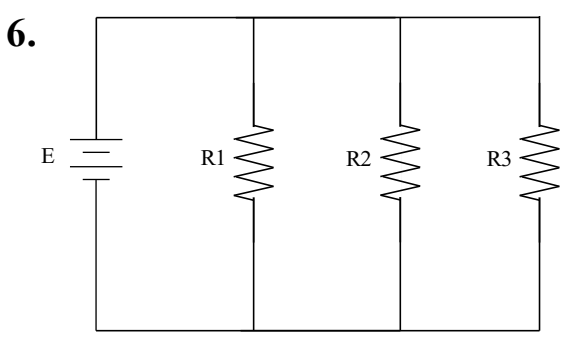$E = 12 \text{ volts}$ $R2 = 12 \text{ ohms}$
 $I_T = 4 \text{ amperes}$ $R3 = \underline{\hspace{2cm}}$
 $R1 = 12 \text{ ohms}$



$E = \underline{\hspace{2cm}}$ $R2 = 24 \text{ ohms}$
 $I_T = 2 \text{ amperes}$ $R3 = 12 \text{ ohms}$
 $R1 = 24 \text{ ohms}$