

Name _____

MATCHING. Choose the item in column 2 that best matches each item in column 1.

- | | | |
|--|---------------------------|----------|
| 1) Resistances add together for total resistance | A) Series circuit | 1) _____ |
| 2) Series circuit current | B) Lowers resistance | 2) _____ |
| 3) Current adds together for total current | C) Parallel circuit | 3) _____ |
| 4) More loads in a series circuit | D) Decreases current | 4) _____ |
| 5) More loads in parallel | E) Voltage drop test | 5) _____ |
| 6) Loads in parallel | F) The same at all points | 6) _____ |
| 7) A dynamic test for resistance | G) Increases current | 7) _____ |
| 8) Loads in series | H) Increases resistance | 8) _____ |
| | I) Ohmmeter test | |