

Name _____

SHORT ANSWER. Write the word or phrase that best completes each statement or answers the question.

1) What do the terminals of a typical ISO relay mean?

2) What do the circuit numbers shown on schematics usually mean?

3) What is used to control voltage spikes inside a relay

4) How can a tone generator be used to locate a short circuit?

5) What is the difference between a relay and a solenoid?
