

Name _____

SHORT ANSWER. Write the word or phrase that best completes each statement or answers the question.

1) What are the steps necessary to replace a starter?

2) What are typical starter amperage draw for four-, six-, and eight-cylinder engines?

3) What could be the cause of excessive starter current draw

4) What are the steps taken to perform a voltage drop test of the cranking circuit?

5) What are the steps involved in the diagnosis of a fault in the cranking circuit?
