

Name \_\_\_\_\_

**SHORT ANSWER. Write the word or phrase that best completes each statement or answers the question.**

1) What are the component parts of a typical alternator?

---

---

2) What is the purpose of an OAP or OAD?

---

---

3) How is AC voltage inside the alternator changed to DC voltage at the output terminal?

---

---

4) How can a small electronic voltage regulator control the output of a typical 100-ampere alternator?

---

---

5) How is the computer is used to control an alternator?

---

---