

Electrical Circuits

Meets ASE Task: Not specified.

Name: _____ Date: _____ Time on Task: _____

Make/Model/Year: _____ VIN: _____

Evaluation (Enter number from 4, 3, 2, 1) : _____

1. Draw a complete electrical circuit and label all the parts.

2. What is an open circuit?

3. Describe the difference between a short-to-voltage and a short-to-ground.

4. State Ohm's Law

5. State Watt's Law
