

# Parallel Circuit Worksheet #1

Meets ASE Task: A6 – A-4 – P-1

Name: \_\_\_\_\_ Date: \_\_\_\_\_ Time on Task: \_\_\_\_\_

Make/Model/Year: \_\_\_\_\_ VIN: \_\_\_\_\_

Evaluation (Enter number from 4, 3, 2, 1) : \_\_\_\_\_

1. Determine the missing value for each parallel circuit.

