

Series-Parallel Circuit Worksheet #1

Meets ASE Task: A6 – A-4 – P-1

Name: _____ Date: _____ Time on Task: _____

Make/Model/Year: _____ VIN: _____

Evaluation (Enter number from 4, 3, 2, 1) : _____

1. Determine the missing value for each series-parallel circuit.

