

# Diagnose Electrical/Electronic Circuits

Meets ASE Task: A6 – A-9 – P-1

Name: \_\_\_\_\_ Date: \_\_\_\_\_ Time on Task: \_\_\_\_\_

Make/Model/Year: \_\_\_\_\_ VIN: \_\_\_\_\_

Evaluation (Enter number from 4, 3, 2, 1) : \_\_\_\_\_

1. Check service information to determine the specified diagnosis procedures to follow for a slowly operating wiper motor. This circuit is a:
- Series
  - Parallel
  - Series-Parallel
2. One tail light is dim; all other exterior lighting operates normally. Check service information to determine the specified diagnostic procedure to follow for a dim tail light.
- Series
  - Parallel
  - Series-Parallel
3. Check service information to determine the specified diagnostic procedure to follow to correctly diagnose a fault in a blower motor circuit.

---

---

---

